

# Laboratory Six MOSFET

**Javier Jesús Macossay-Hernández**  
**EE348L – Electronic Circuits**  
**University of Southern California**  
**Professor Susan Schober**

## Introduction


MOSFETs is a type of transistor used for amplifying or switching electronic signals. Additionally, small signal analysis is done to have a guess of the transistor's behavior and to calculate the gain on the simple transistor amplifiers. Two amplifiers were built, common-source and common-drain amplifiers. Small signals resulting from large signals input and load influences were analyzed as well.

## Exercise 1

### Procedure

On Exercise 1, the following circuit was built. The gain was calculated for  $I_d = 1\text{mA}$  and the input signal to the circuit was a sinusoidal signal of 50 mV with 10 kHz.  $V_{dd} = 5\text{V}$ .

### Data

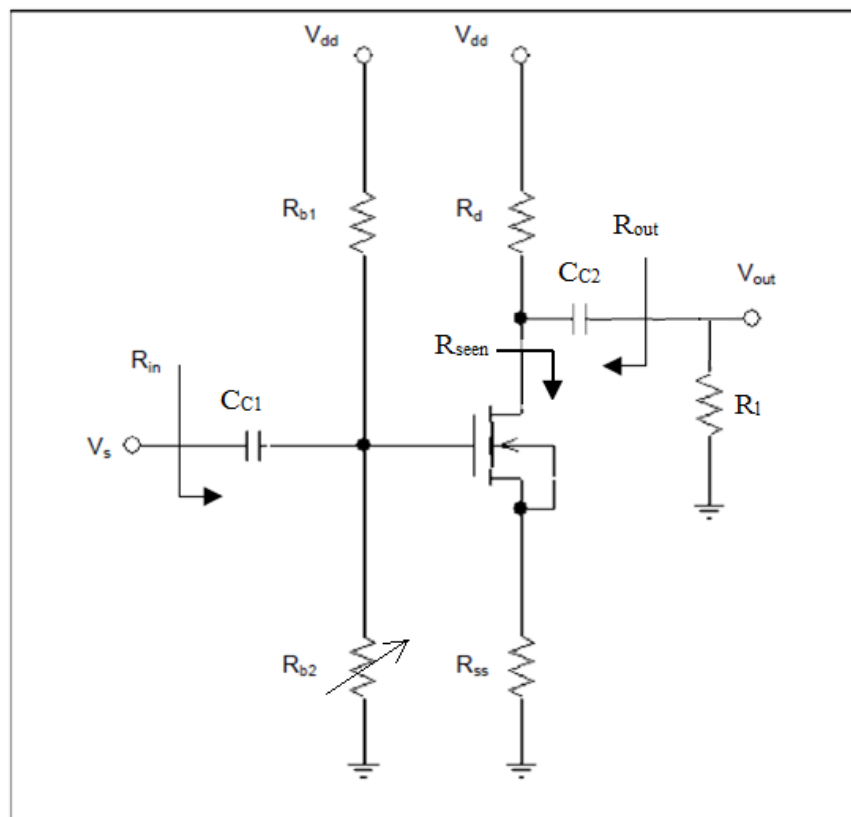

Circuit Schematic

|        |                |                   |                   |                   |                  |                  |
|--------|----------------|-------------------|-------------------|-------------------|------------------|------------------|
|        | $R_D (\Omega)$ | $R_{SS} (\Omega)$ | $R_{B1} (\Omega)$ | $R_{B2} (\Omega)$ | $C_{C1} (\mu F)$ | $C_{C2} (\mu F)$ |
| Values | 1487           | 501               | 21620             | 25060             | 5 $\mu F$        | 5 $\mu F$        |

### Questions

The gain is larger than the one from the calculations and SPICE simulations because we used a simplified model for the hand analysis.

### Discussion

From the actual circuit, the  $V_{in} = 130$  mV peak-to-peak voltage and a  $V_{out} = 480$  mV. As a result, the gain is 3.63.

### Exercise 2

#### Procedure

On Exercise 2, the gain from Exercise 1 was doubled. The theoretical equation for gain used is:

$$A_v = -\frac{gm R_d}{1 + gm R_{ss}}$$

### Discussion

By analyzing the equation,  $R_d$  should be incremented or  $R_{ss}$  should be decreased. In order to obtain a gain twice the value from Exercise 1, 7.18, we will make  $R_{ss} = 110 \Omega$  to obtain a  $V_{out}$  of 934 mV.

### Exercise 3

#### Procedure.

On Exercise 3, we would use circuit from Exercise 1. The gain was calculated using when different values for resistances were used. 100 k $\Omega$ , 10 k $\Omega$ , 1k $\Omega$ , and 100  $\Omega$ .

### Data

| Theory Value for R ( $\Omega$ ) | Real Value for R ( $\Omega$ ) | Gain |
|---------------------------------|-------------------------------|------|
| 100k                            | 98.67k                        | 3.44 |
| 10k                             | 9.89k                         | 3.44 |
| 1k                              | 995                           | 1.29 |
| 100                             | 99.3                          | 0.5  |

### Questions

The results of this analysis match with the results of pre-lab Exercise 4, therefore they confirm our expectations.

### Discussion


The gain gets influenced as the value of  $R_L$  gets closer to the value of  $R_D$ . As  $R_D$  decreases, the resistance goes to zero. As a result, the gain dropped.

## Exercise 4

### Procedure

On Exercise 4, the following circuit was built. The gain was calculated for  $I_d = 1\text{mA}$  and the input signal to the circuit was a sinusoidal signal of 50 mV with 10 kHz.  $V_{dd} = 5\text{V}$ .

### Data

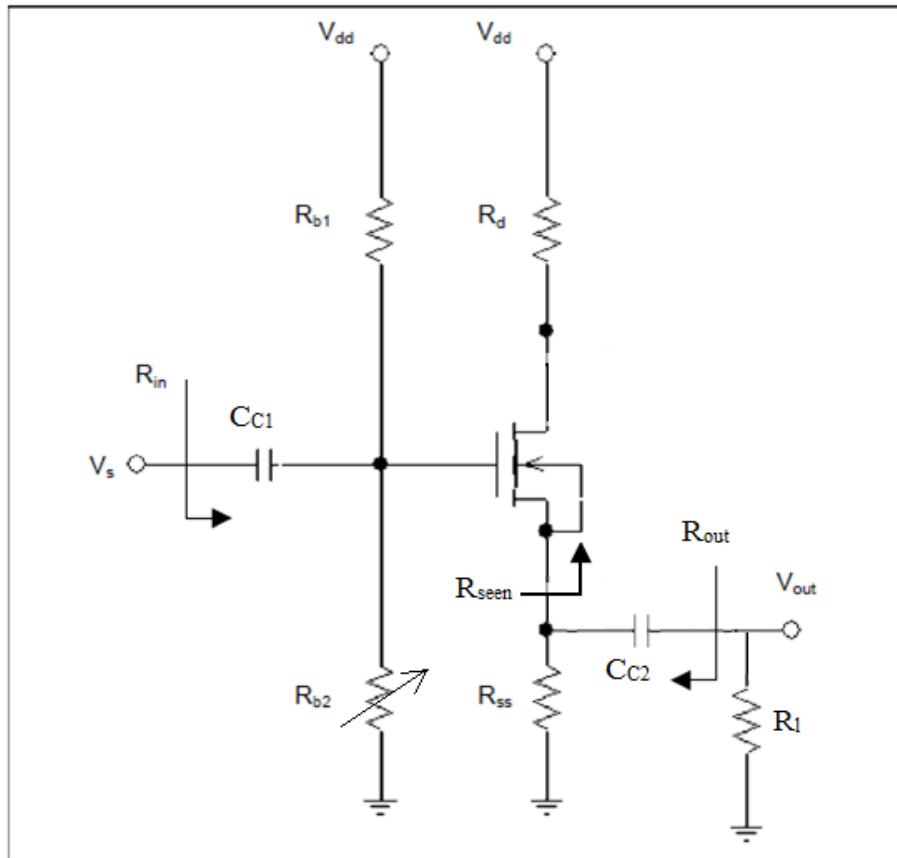

|        | $R_D (\Omega)$ | $R_{SS} (\Omega)$ | $R_{B1} (\Omega)$ | $R_{B2} (\Omega)$ | $C_{C1} (\mu\text{F})$ | $C_{C2} (\mu\text{F})$ |
|--------|----------------|-------------------|-------------------|-------------------|------------------------|------------------------|
| Values | 1487           | 501               | 21620             | 27100             | 5 $\mu\text{F}$        | 5 $\mu\text{F}$        |

### Questions

The result, in this case the gain, yields to what expected from the circuit.

### Discussion

In this exercise  $V_s = 130\text{ mV}$  peak-to-peak and  $V_{out} = 142\text{ mV}$ . As a result, gain is equal to 1.09.

---

## Exercise 5

### Procedure

On Exercise 5, the load resistance was increased from 100  $\Omega$  to 100 k $\Omega$ . As resistance was increased, the gain increased because the resistance becomes closer to become an open circuit. Therefore, it affects the gain less.

### Data

| Theory Value for R ( $\Omega$ ) | Real Value for R ( $\Omega$ ) | Gain  |
|---------------------------------|-------------------------------|-------|
| 100k                            | 98.67k                        | 1.016 |
| 10k                             | 9.89k                         | 1.048 |
| 1k                              | 995                           | 1.033 |
| 100                             | 99.3                          | 0.613 |

### Questions

The result yields to what expected from the circuit.

### Discussion

For  $R_L$  smaller than  $R_{SS}$  the gain drops because it is directly proportional to  $R_{SS} \parallel R_L$ . In the common-drain gain equation,  $R_{SS}$  is replaced by  $R_L$  and  $g_m R_L$  decreases smaller than 1. As a result, the gain drops.

$$A_V = \frac{g_m R_{SS}}{1 + g_m R_{SS}}$$

### Conclusion

The results clearly agree with the objective of the lab that is analyze amplifiers and its concepts. In general, the results obtained from the laboratory experiments yield to the results from the hand calculations and the SPICE simulations because the common-drain and common-source amplifiers behaviors can be considered successful according to the experiments.