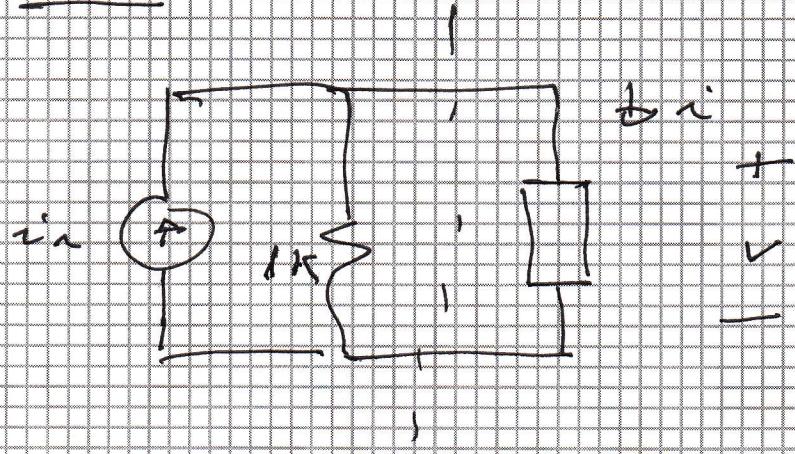


2.6



$$V_Z = \sqrt{V - Z} \text{ mA}$$

$$V = 0 \rightarrow V_Z = i_m$$


$$V = 0 \rightarrow V = i_m (v)$$

$$i_m (\text{mA})$$

$$\leftarrow -V_Z = 7.2 \text{ mA}$$

- Load Line

Characteristic Curve

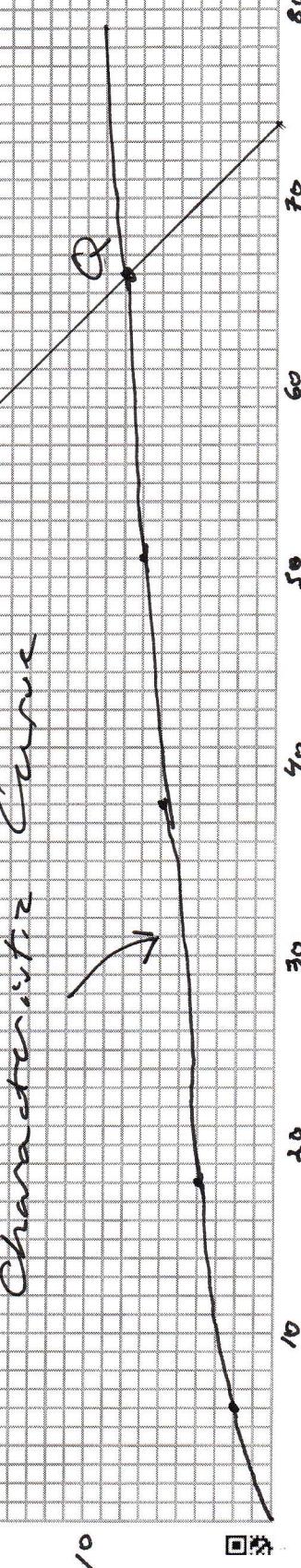

2.28

$$i (\text{mA}) \quad v (\text{volts})$$

0.1	0.713	{	$\Delta v = 0.085$
1.0	0.798		
10	0.809		



This should be
0.882 to be
consistent.
(Text error)


$$\Delta v = 2.3 n \left(\frac{kT}{\sum} \right)$$

$$n = \frac{85 \text{ mV}}{2.3 \times 25.9 \text{ mV}} = 1.43$$

$$1 \text{ mA} \approx I_v \exp \left(\frac{798 \text{ mV}}{1.43 \times 25.9 \text{ mV}} \right)$$

$$\rightarrow I_v = 4.39 \times 10^{-13} \text{ A}$$

2.44

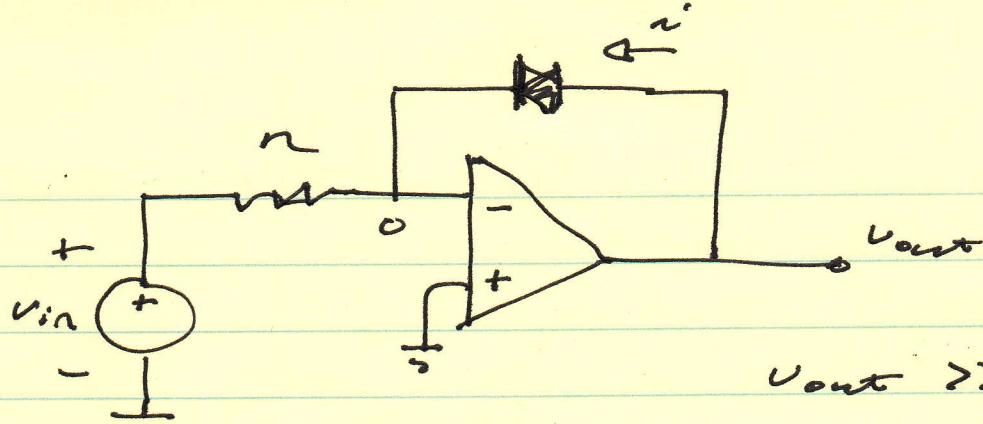


$$v_{out} \gg \frac{kT}{g}$$

$$i \approx I_v e^{\frac{v_{out}}{kT}} = -\frac{v_{in}}{R}$$

$$v_{out} = \frac{kT}{g} \ln \left(\frac{-v_{in}}{I_v R} \right) \quad v_{in} < 0$$

2.45

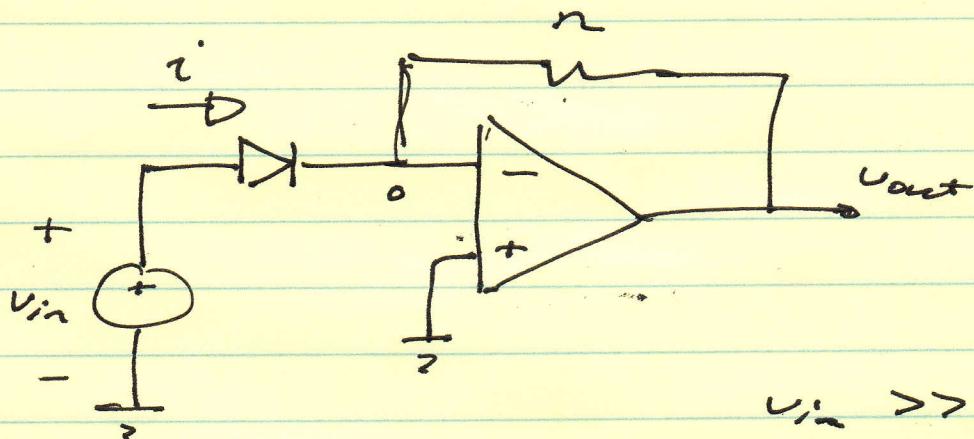


$$v_{in} \gg \frac{kT}{g}$$

$$i \approx I_v e^{\frac{v_{in}}{kT}} = -\frac{v_{out}}{r}$$

$$v_{out} = -I_v R e^{\frac{v_{in}}{kT}} \quad v_{in} > 0$$
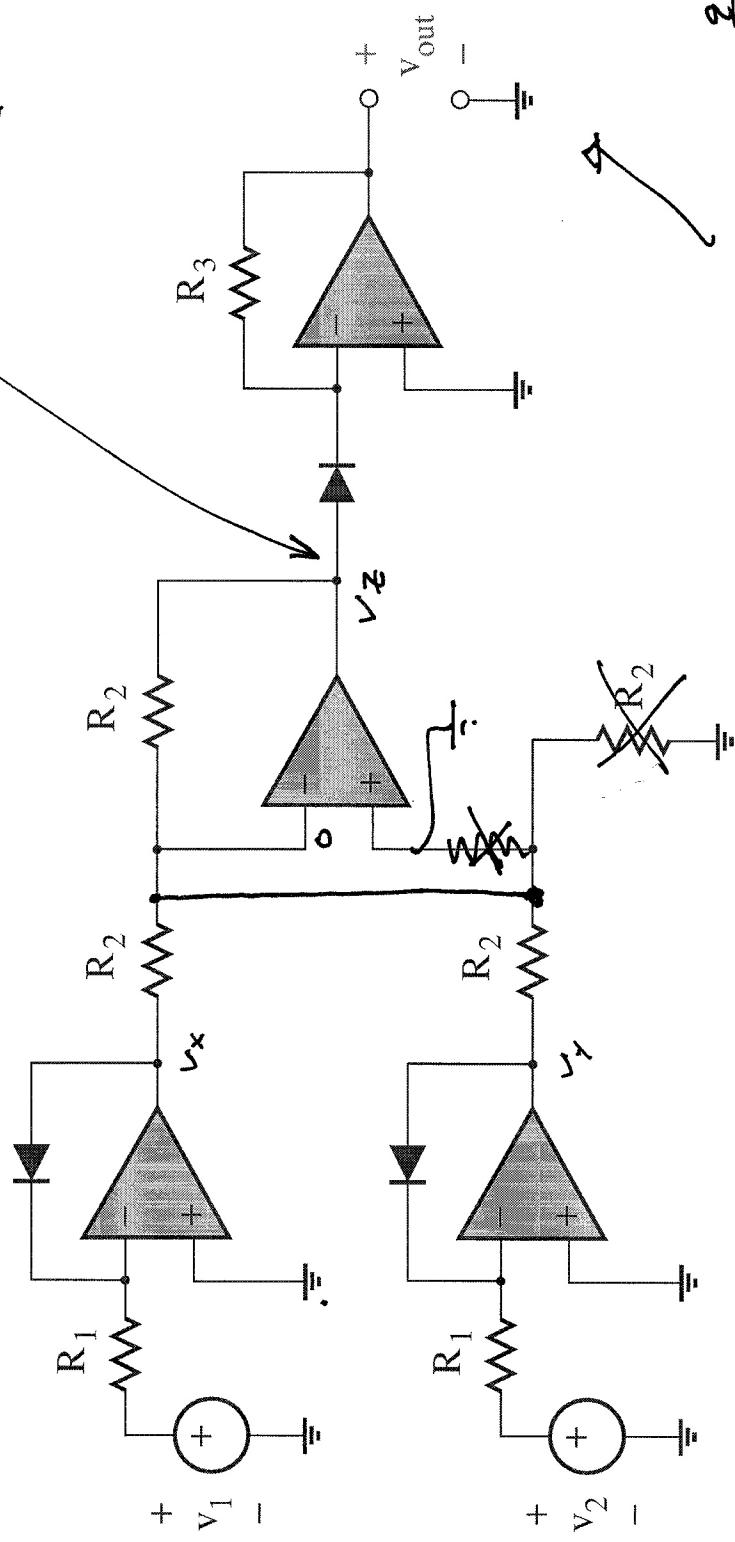
$$v_z = -v_x - v_y \left(\frac{v_1 v_2}{\omega n_i} \right)$$



$$\frac{2 v_{out}}{k \tau}$$

$$v_{out} = -I_v n_i e$$

$$= \frac{v_1 v_2 n_i}{I_v n_i \tau}$$

multisim


$$v_x = k \frac{v_1}{\xi} \ln \left(\frac{-v_1}{\omega n_i} \right)$$

$$v_y = k \frac{v_2}{\xi} \ln \left(\frac{-v_2}{\omega n_i} \right)$$

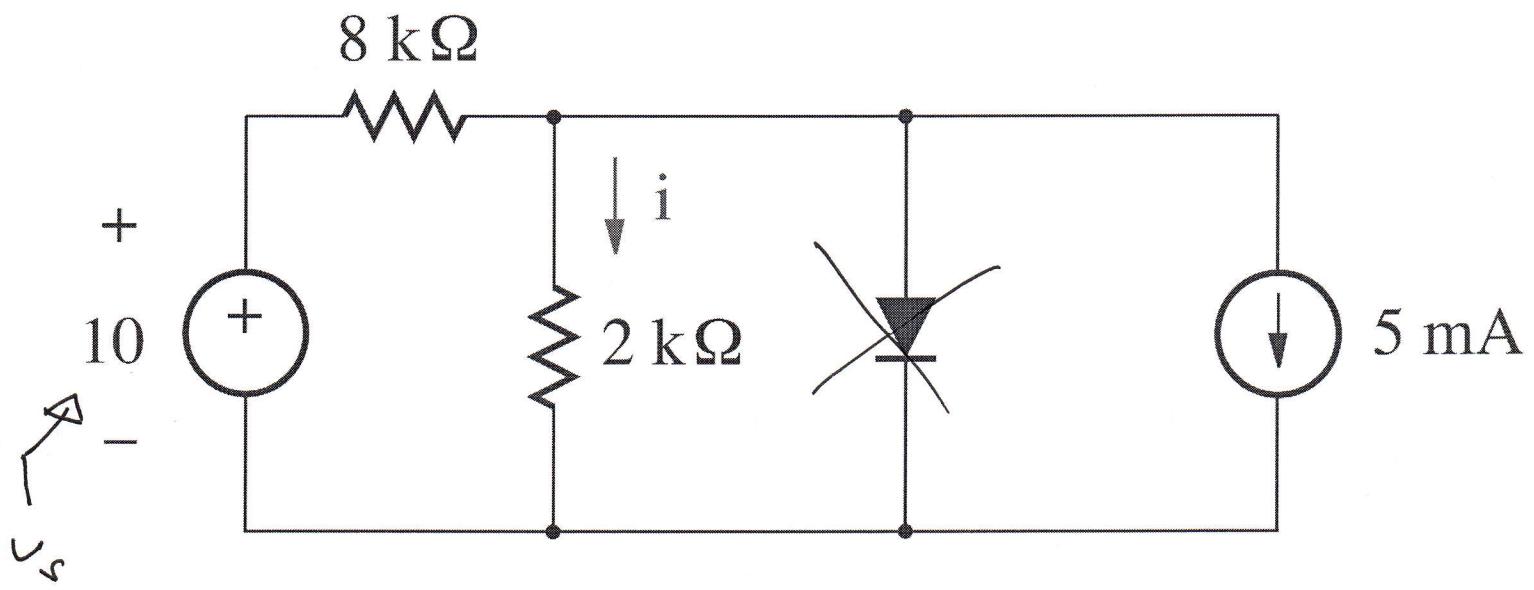3.6

At diode break point, $\frac{v_s}{8} = 5$
 $\rightarrow v_s = 40$ diode on for $v_s > 40$

But $v_s = 10$, so the diode is off.
 \Rightarrow open



superposition

$$i = \frac{10}{10} + (-5) \frac{\frac{1}{2}}{\frac{1}{2} + \frac{1}{8}} = -3 \text{ mA}$$

↑

current
source
off


↑

voltage
source
off

3.10

D₁ breakdown


mark up diagram

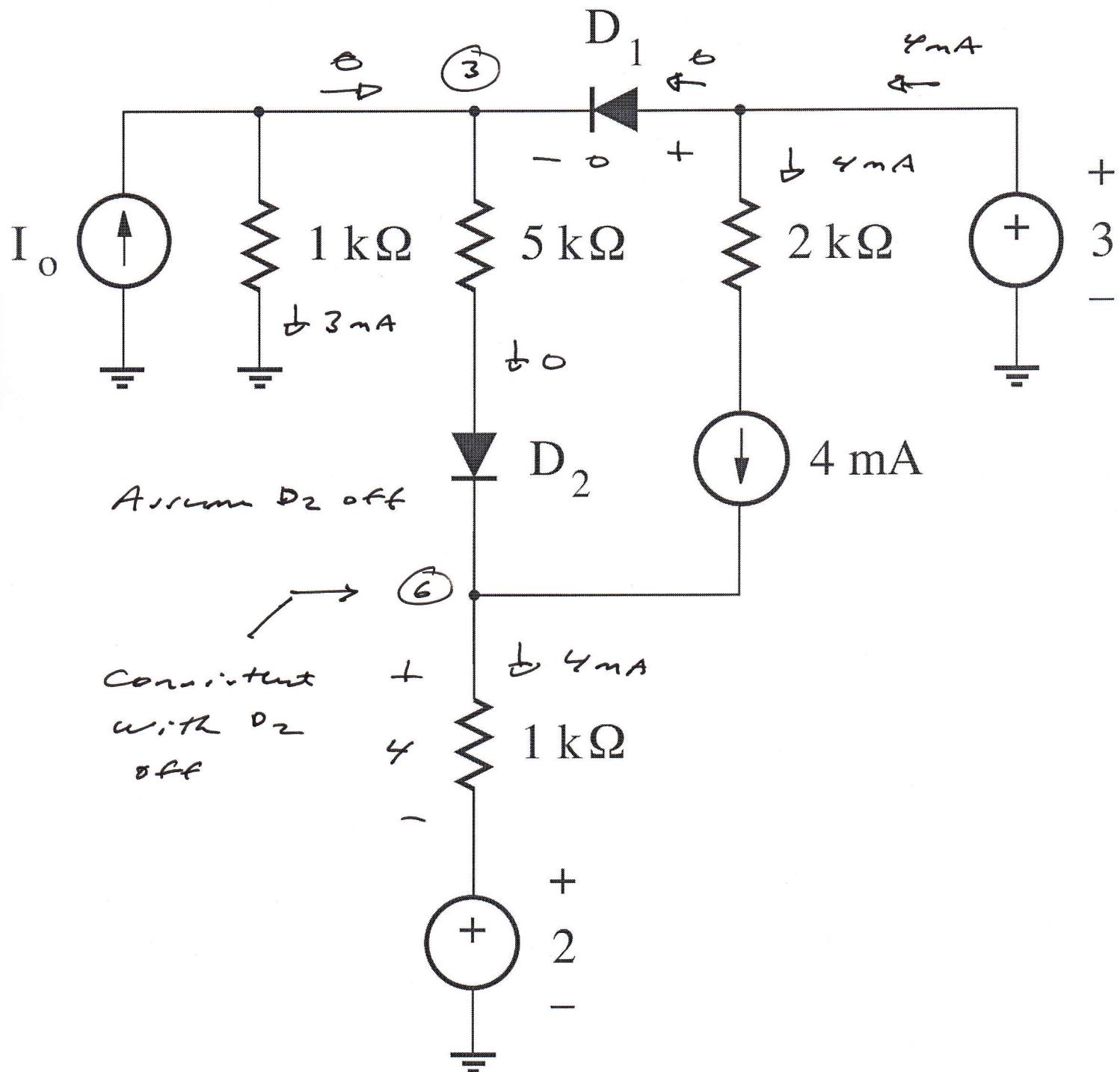

$$I_0 = 3\text{ mA}$$

D_1 on for $I_0 < 3\text{ mA}$


3.10 D_2 breakpoint mark up diagram

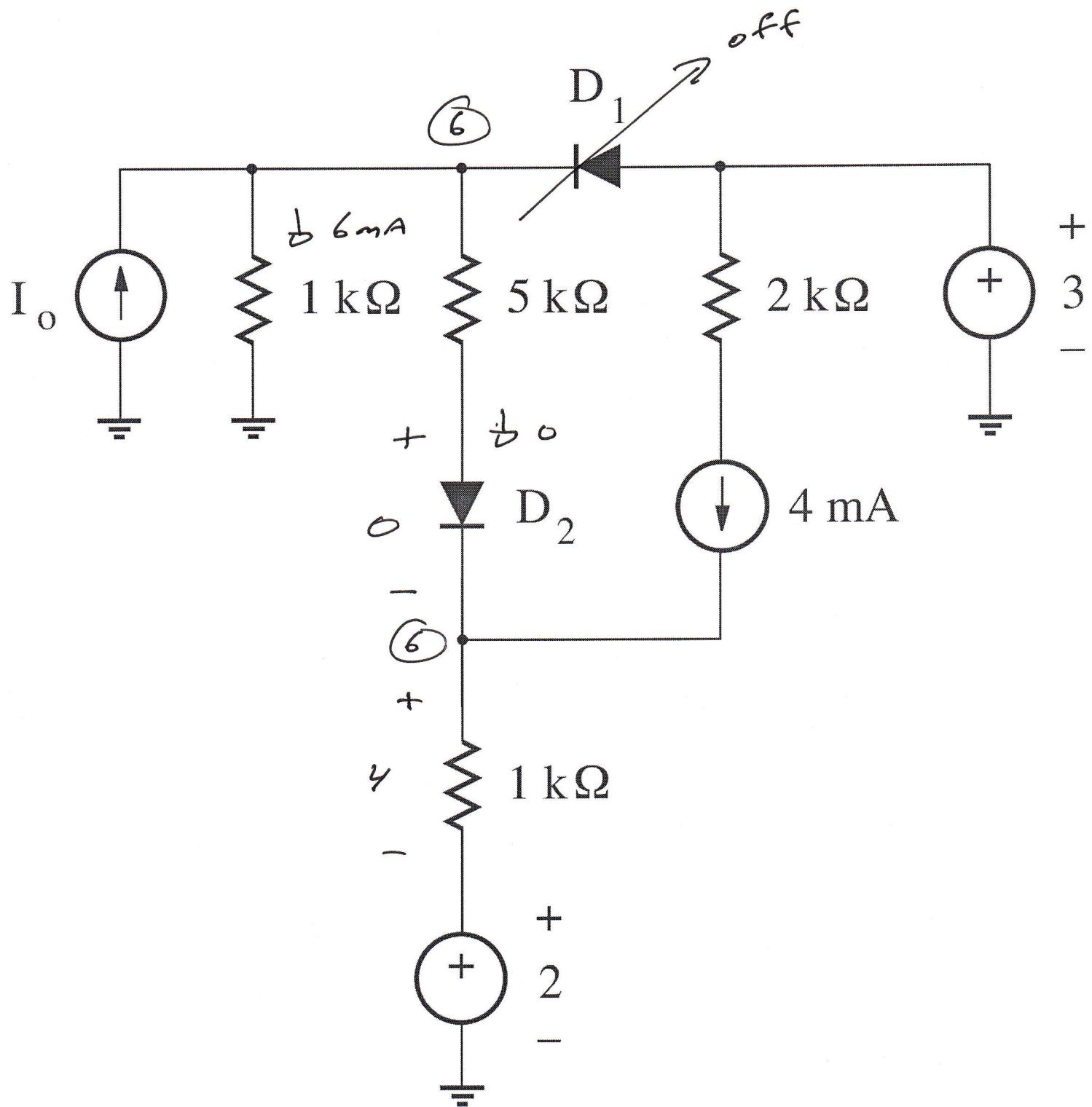

$$I_o = 6 \text{ mA}$$

D_2 on for $I_o > 6 \text{ mA}$

3.21 D, breakpoint

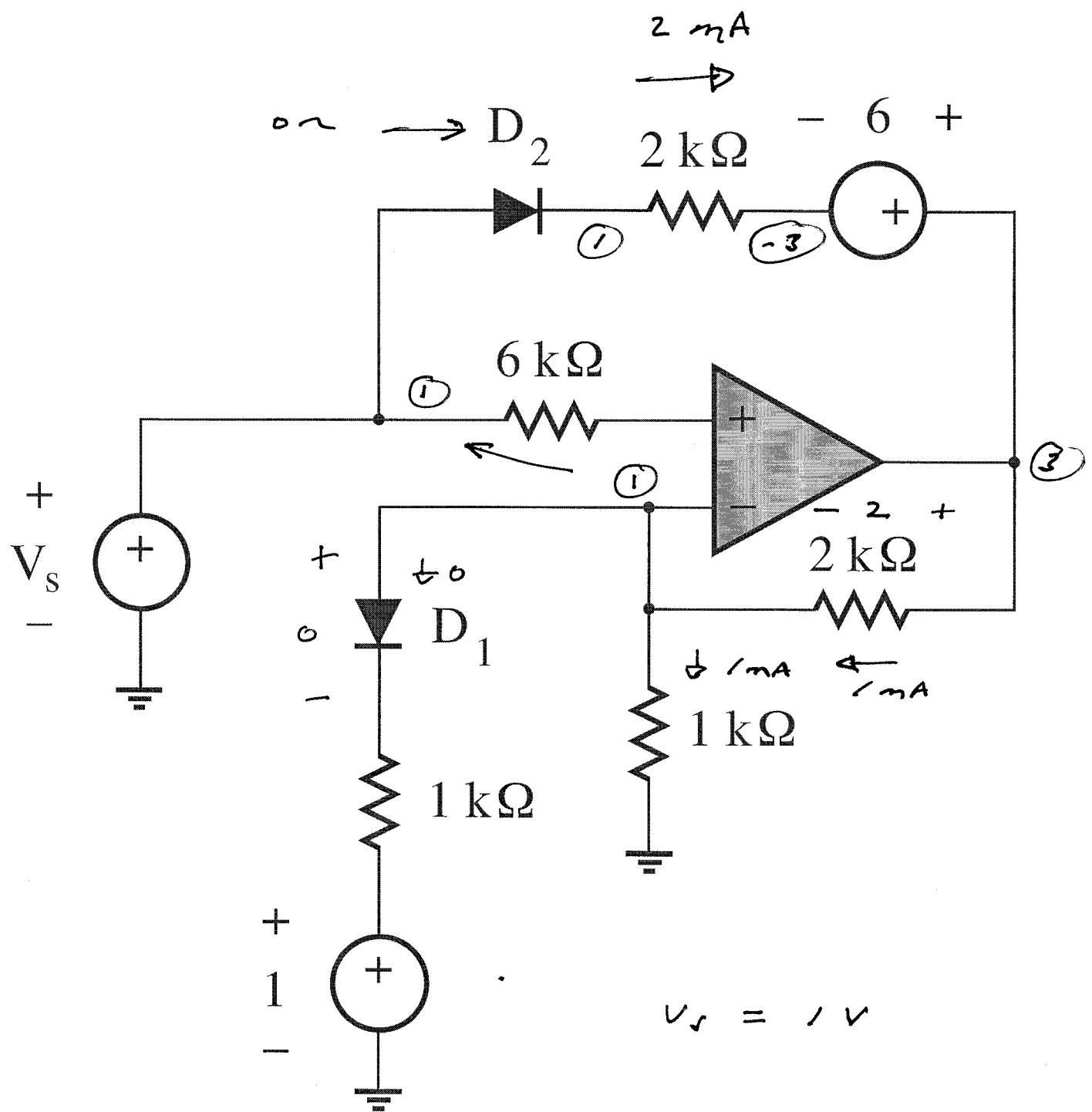

D_2 breakpoint

