


University of Southern California
Ming Hsieh Department of Electrical Engineering
EE 348L - Electronic Circuits
Spring 2016

Homework 3 Solutions

At the end of the chapter complete the following 12 problems: 4.4, ~~4.9~~, ~~4.10~~, ~~4.17~~, ~~4.20~~, ~~4.26~~, ~~4.27~~, ~~4.28~~, ~~4.59~~, ~~4.86~~, ~~4.87~~, and ~~4.90~~.


4.4

(a)

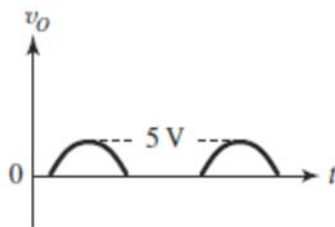


$$V_{p+} = 5 \text{ V} \quad V_{p-} = 0 \text{ V} \quad f = 1 \text{ kHz}$$

(b)

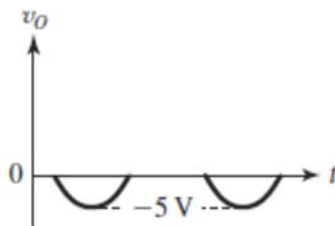

$$V_{p+} = 0 \text{ V} \quad V_{p-} = -5 \text{ V} \quad f = 1 \text{ kHz}$$


(c)

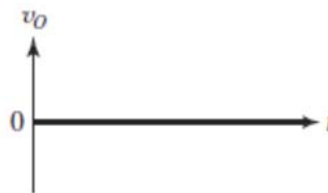

$$v_O = 0 \text{ V}$$

Neither D_1 nor D_2 conducts, so there is no output.


(d)

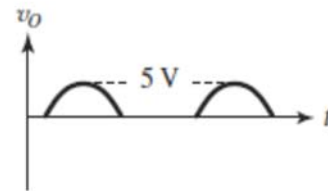

$$V_{p+} = 5 \text{ V}, \quad V_{p-} = 0 \text{ V}, \quad f = 1 \text{ kHz}$$

Both D_1 and D_2 conduct when $v_I > 0$


(e)

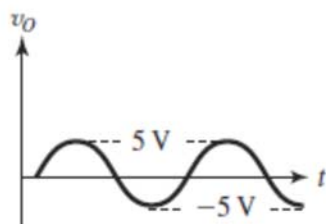

$$V_{p+} = 5 \text{ V}, \quad V_{p-} = -5 \text{ V}, \quad f = 1 \text{ kHz}$$

D_1 conducts when $v_I > 0$ and D_2 conducts when $v_I < 0$. Thus the output follows the input.


(f)

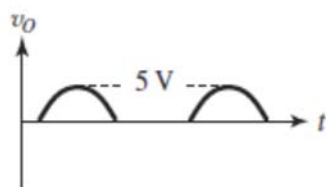

$$V_{p+} = 5 \text{ V}, \quad V_{p-} = 0 \text{ V}, \quad f = 1 \text{ kHz}$$

D_1 is cut off when $v_I < 0$


(g)

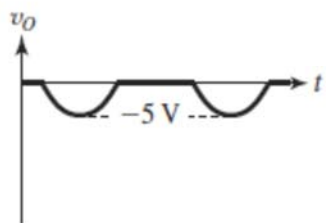

$$V_{p+} = 0 \text{ V}, \quad V_{p-} = -5 \text{ V}, \quad f = 1 \text{ kHz}$$


D_1 shorts to ground when $v_I > 0$ and is cut off when $v_I < 0$ whereby the output follows v_I .

(h)

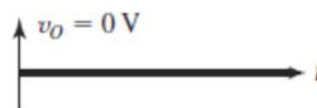

$v_O = 0 \text{ V}$ ~ The output is always shorted to ground as D_1 conducts when $v_I > 0$ and D_2 conducts when $v_I < 0$.

(i)

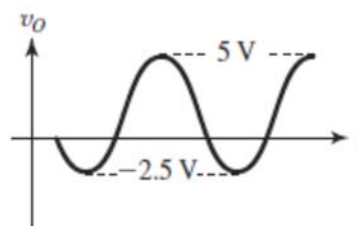


$$V_{p+} = 5 \text{ V}, \quad V_{p-} = -2.5 \text{ V}, \quad f = 1 \text{ kHz}$$

When $v_I > 0$, D_1 is cut off and v_O follows v_I .

When $v_I < 0$, D_1 is conducting and the circuit becomes a voltage divider where the negative peak is

$$\frac{1 \text{ k}\Omega}{1 \text{ k}\Omega + 1 \text{ k}\Omega} \times -5 \text{ V} = -2.5 \text{ V}$$

(j)

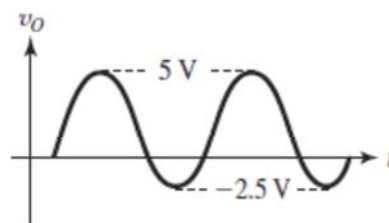


$$V_{p+} = 5 \text{ V}, \quad V_{p-} = -2.5 \text{ V}, \quad f = 1 \text{ kHz}$$

When $v_I > 0$, the output follows the input as D_1 is conducting.

When $v_I < 0$, D_1 is cut off and the circuit becomes a voltage divider.

(k)

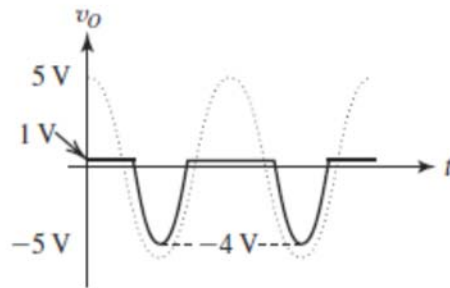


$$V_{p+} = 1 \text{ V}, \quad V_{p-} = -4 \text{ V}, \quad f = 1 \text{ kHz}$$

When $v_I > 0$, D_1 is cut off and D_2 is conducting.
The output becomes 1 V.

When $v_I < 0$, D_1 is conducting and D_2 is cut off.
The output becomes:

$$v_O = v_I + 1 \text{ V}$$


4.9

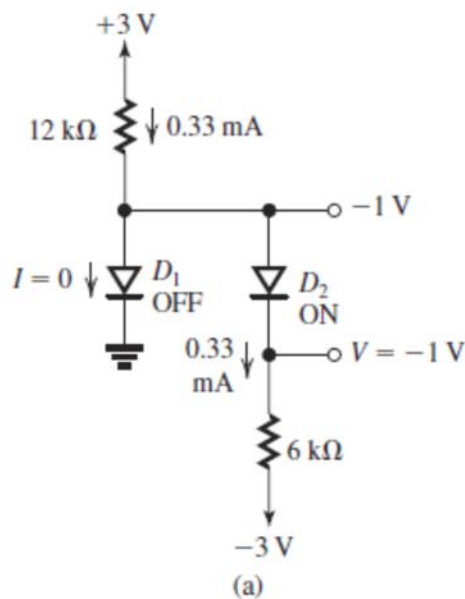

(a) If we assume that both D_1 and D_2 are conducting, then $V = 0 \text{ V}$ and the current in D_2 will be $[0 - (-3)]/6 = 0.5 \text{ mA}$. The current in the 12 kΩ will be $(3 - 0)/12 = 0.25 \text{ mA}$. A node equation at the common anodes node yields a negative current in D_1 . It follows that our assumption is wrong and D_1 must be off. Now making the assumption that D_1 is off and D_2 is on, we obtain the results shown in Fig. (a):

$$I = 0$$

$$V = -1 \text{ V}$$


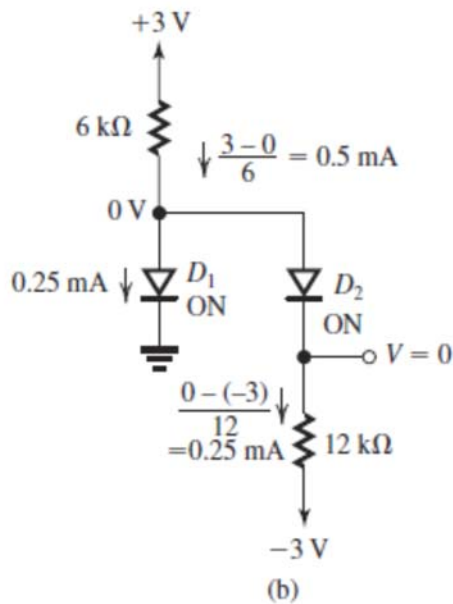


(b) In (b), the two resistors are interchanged. With some reasoning, we can see that the current supplied through the 6-k Ω resistor will exceed that drawn through the 12-k Ω resistor, leaving sufficient current to keep D_1 conducting. Assuming that D_1 and D_2 are both conducting gives the results shown in Fig. (b):

$$I = 0.25 \text{ mA}$$

$$V = 0 \text{ V}$$

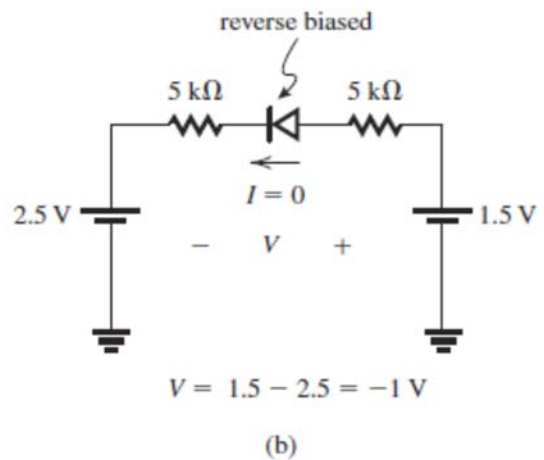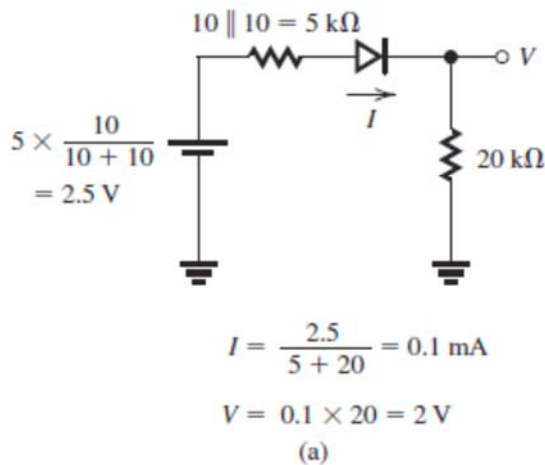4.10 The analysis is shown on the circuit diagrams below.



Thus

$$V_T = 8.62 \times 10^{-5} \times (273 + x^\circ\text{C}), \text{ V}$$

$$4.17 \quad V_T = \frac{kT}{q}$$

where

$$k = 1.38 \times 10^{-23} \text{ J/K} = 8.62 \times 10^{-5} \text{ eV/K}$$

$$T = 273 + x^\circ\text{C}$$

$$q = 1.60 \times 10^{-19} \text{ C}$$

$x [^\circ\text{C}]$	$V_T [\text{mV}]$
-55	18.8
0	23.5
+55	28.3
+125	34.3

for $V_T = 25 \text{ mV}$ at 17°C

$$4.20 \quad I = I_S e^{V_D/V_T}$$

$$10^{-3} = I_S e^{0.7/V_T} \quad (1)$$

For $V_D = 0.71 \text{ V}$,

$$I = I_S e^{0.71/V_T} \quad (2)$$

Combining (1) and (2) gives

$$\begin{aligned} I &= 10^{-3} e^{(0.71 - 0.7)/0.025} \\ &= 1.49 \text{ mA} \end{aligned}$$

For $V_D = 0.8 \text{ V}$,

$$I = I_S e^{0.8/V_T} \quad (3)$$

Combining (1) and (3) gives

$$\begin{aligned} I &= 10^{-3} \times e^{(0.8 - 0.7)/0.025} \\ &= 54.6 \text{ mA} \end{aligned}$$

Similarly, for $V_D = 0.69 \text{ V}$ we obtain

$$\begin{aligned} I &= 10^{-3} \times e^{(0.69 - 0.7)/0.025} \\ &= 0.67 \text{ mA} \end{aligned}$$

and for $V_D = 0.6 \text{ V}$ we have


$$\begin{aligned} I &= 10^{-3} e^{(0.6 - 0.7)/0.025} \\ &= 18.3 \text{ } \mu\text{A} \end{aligned}$$

To increase the current by a factor of 10, V_D must be increased by ΔV_D ,

$$10 = e^{\Delta V_D/0.025}$$

$$\Rightarrow \Delta V_D = 0.025 \ln 10 = 57.6 \text{ mV}$$

4.26

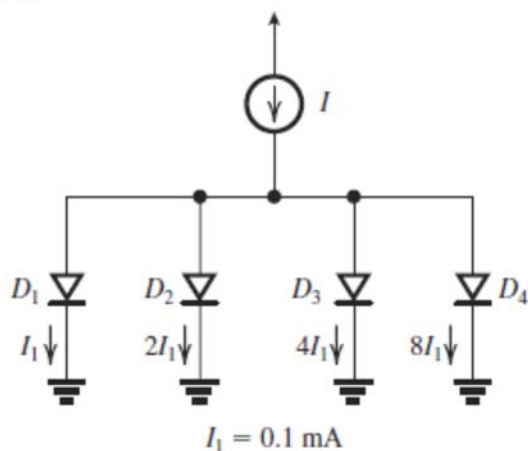

The junction areas of the four diodes must be related by the same ratios as their currents, thus

$$A_4 = 2A_3 = 4A_2 = 8A_1$$

With $I_1 = 0.1 \text{ mA}$,

$$I = 0.1 + 0.2 + 0.4 + 0.8 = 1.5 \text{ mA}$$

4.27 We can write a node equation at the anodes:

$$I_{D2} = I_1 - I_2 = 7 \text{ mA}$$

$$I_{D1} = I_2 = 3 \text{ mA}$$

We can write the following equation for the diode voltages:

$$V = V_{D2} - V_{D1}$$

If D_2 has saturation current I_S , then D_1 , which is 10 times larger, has saturation current $10I_S$. Thus we can write

$$I_{D2} = I_S e^{V_{D2}/V_T}$$

$$I_{D1} = 10I_S e^{V_{D1}/V_T}$$

Taking the ratio of the two equations above, we have

$$\frac{I_{D2}}{I_{D1}} = \frac{7}{3} = \frac{1}{10} e^{(V_{D2}-V_{D1})/V_T} = \frac{1}{10} e^{V/V_T}$$

$$\Rightarrow V = 0.025 \ln\left(\frac{70}{3}\right) = 78.7 \text{ mV}$$

To instead achieve $V = 60 \text{ mV}$, we need

$$\frac{I_{D2}}{I_{D1}} = \frac{I_1 - I_2}{I_2} = \frac{1}{10} e^{0.06/0.025} = 1.1$$

Solving the above equation with I_1 still at 10 mA , we find $I_2 = 4.76 \text{ mA}$.

4.28 We can write the following node equation at the diode anodes:

$$I_{D2} = 10 \text{ mA} - V/R$$

$$I_{D1} = V/R$$

We can write the following equation for the diode voltages:

$$V = V_{D2} - V_{D1}$$

We can write the following diode equations:

$$I_{D2} = I_S e^{V_{D2}/V_T}$$

$$I_{D1} = I_S e^{V_{D1}/V_T}$$

Taking the ratio of the two equations above, we have

$$\frac{I_{D2}}{I_{D1}} = \frac{10 \text{ mA} - V/R}{V/R} = e^{(V_{D2}-V_{D1})/V_T} = e^{V/V_T}$$

To achieve $V = 50 \text{ mV}$, we need

$$\frac{I_{D2}}{I_{D1}} = \frac{10 \text{ mA} - 0.05/R}{0.05/R} = e^{0.05/0.025} = 7.39$$

Solving the above equation, we have

$$R = 42 \, \Omega$$

$$4.59 \quad V_Z = V_{Z0} + I_{ZT} r_z$$

$$(a) \quad 10 = 9.6 + 0.05 \times r_z$$

$$\Rightarrow r_z = 8 \, \Omega$$

$$\text{For } I_Z = 2I_{ZT} = 100 \text{ mA,}$$

$$V_Z = 9.6 + 0.1 \times 8 = 10.4 \text{ V}$$

$$P = 10.4 \times 0.1 = 1.04 \text{ W}$$

$$(b) \quad 9.1 = V_{Z0} + 0.01 \times 30$$

$$\Rightarrow V_{Z0} = 8.8 \text{ V}$$

$$\text{At } I_Z = 2I_{ZT} = 20 \text{ mA,}$$

$$V_Z = 8.8 + 0.02 \times 30 = 9.4 \text{ V}$$

$$P = 9.4 \times 20 = 188 \text{ mW}$$

$$(c) \quad 6.8 = 6.6 + I_{ZT} \times 2$$

$$\Rightarrow I_{ZT} = 0.1 \text{ A}$$

$$\text{At } I_Z = 2I_{ZT} = 0.2 \text{ A,}$$

$$V_Z = 6.6 + 0.2 \times 2 = 7 \text{ V}$$

$$P = 7 \times 0.2 = 1.4 \text{ W}$$

$$(d) \quad 18 = 17.6 + 0.005 \times r_z$$

$$\Rightarrow r_z = 80 \, \Omega$$

$$\text{At } I_Z = 2I_{ZT} = 0.01 \text{ A,}$$

$$V_Z = 17.6 + 0.01 \times 80 = 18.4 \text{ V}$$

$$P = 18.4 \times 0.01 = 0.184 \text{ W} = 184 \text{ mW}$$

$$(e) \quad 7.5 = V_{Z0} + 0.2 \times 1.5$$

$$\Rightarrow V_{Z0} = 7.2 \text{ V}$$

$$\text{At } I_Z = 2I_{ZT} = 0.4 \text{ A,}$$


$$V_Z = 7.2 + 0.4 \times 1.5 = 7.8 \text{ V}$$

$$P = 7.8 \times 0.4 = 3.12 \text{ W}$$

4.86 $v_I > 0$: D_1 conducts and D_2 cutoff

$v_I < 0$: D_1 cutoff,

D_2 conducts $\sim \frac{v_O}{v_I} = -1$

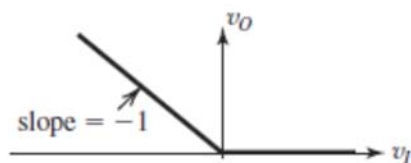

(a) $v_I = +1$ V

$v_O = 0$ V

$v_A = -0.7$ V

Keeps D_2 off so no current flows through R

$\Rightarrow v_- = 0$ V

Virtual ground as feedback loop is closed through D_1

(b) $v_I = +3$ V

$v_O = 0$ V

$v_A = -0.7$ V

$v_- = 0$ V

(c) $v_I = -1$ V

$v_O = +1$ V

$v_A = 1.7$ V

$v_- = 0$ V

\sim Virtual ground as negative feedback loop is closed through D_2 and R .

(d) $v_I = -3$ V $\Rightarrow v_O = +3$ V

$v_A = +3.7$ V

$v_- = 0$ V

4.87 (a) See figure (a) on next page. For $v_I \leq 3.5$ V, $i = 0$ and $v_O = v_I$. At $v_I = 3.5$ V, the diode begins to conduct. At $v_O = 3.7$ V, the diode is conducting $i = 1$ mA and thus

$$v_I = v_O + i \times 1 \text{ k}\Omega = 4.7 \text{ V}$$

For $v_I > 4.7$ V the diode current increases but the diode voltage remains constant at 0.7 V, thus v_O flattens and v_O vs. v_I becomes a horizontal line.

In practice, the diode voltage increases slowly and the line will have a small nonzero slope.

(b) See figure (b) on next page. Here $v_O = v_I$ for $v_I \geq 2.5$ V. At $v_I = 2.5$ V, $v_O = 2.5$ V and the diode begins to conduct. The diode will be conducting 1 mA and exhibiting a drop of 0.7 at $v_O = 2.3$ V. The corresponding value of v_I



$$v_I = v_O - iR = 2.3 - 1 \times 1 = +1.3 \text{ V}$$


As v_I decreases below 1.3 V, the diode current increases, but the diode voltage remains constant at 0.7 V. Thus v_O flattens at about 2.3 V.

(c) See figure (c) on next page. For $v_I \leq -2.5$ V, the diode is off, and $v_O = v_I$. At $v_I = -2.5$ V the diode begins to conduct and its current reaches 1 mA at $v_I = -1.3$ V (corresponding to $v_O = -2.3$ V). As v_I further increases, the diode current increases but its voltage remains constant at 0.7 V. Thus v_O flattens, as shown.


(d) See figure (d) on next page.

These figures belong to Problem 4.87.

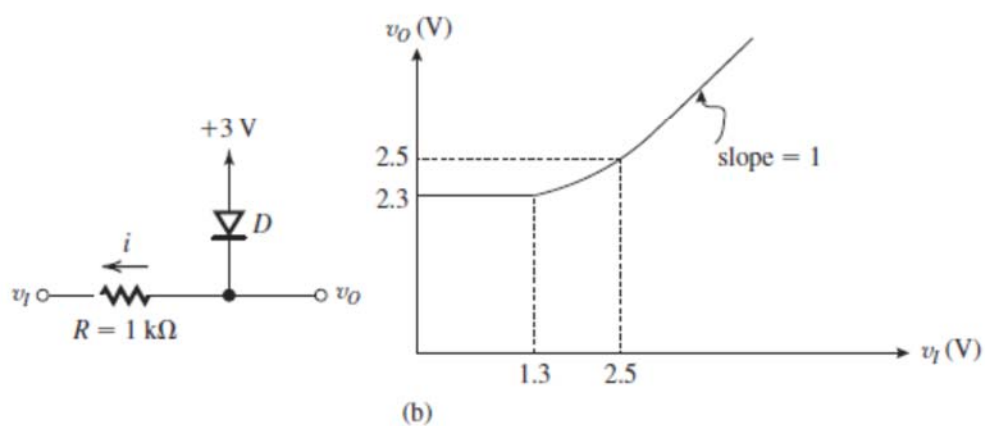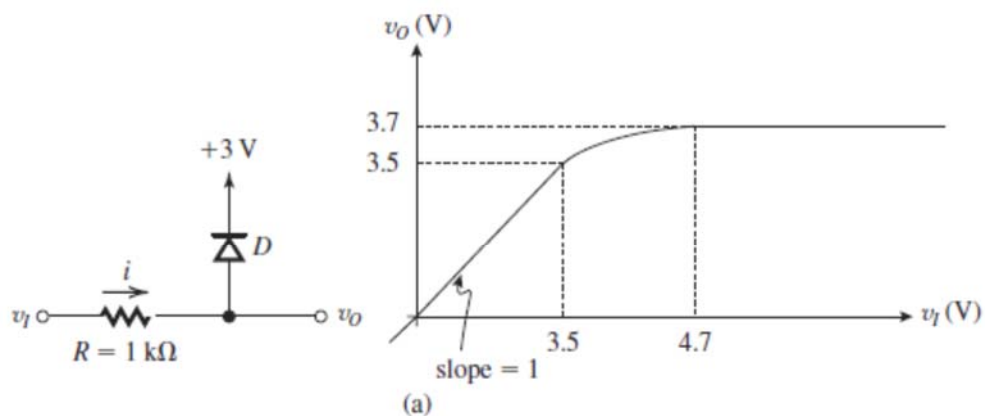

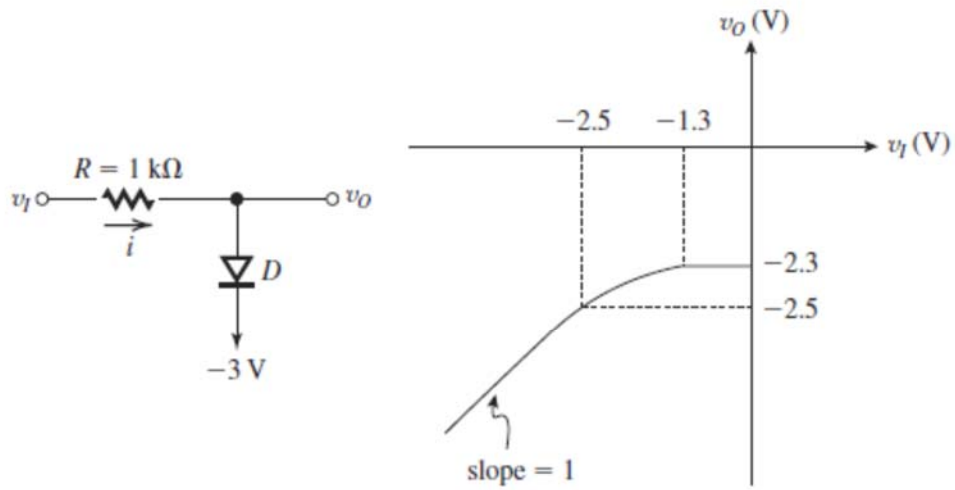


(c)

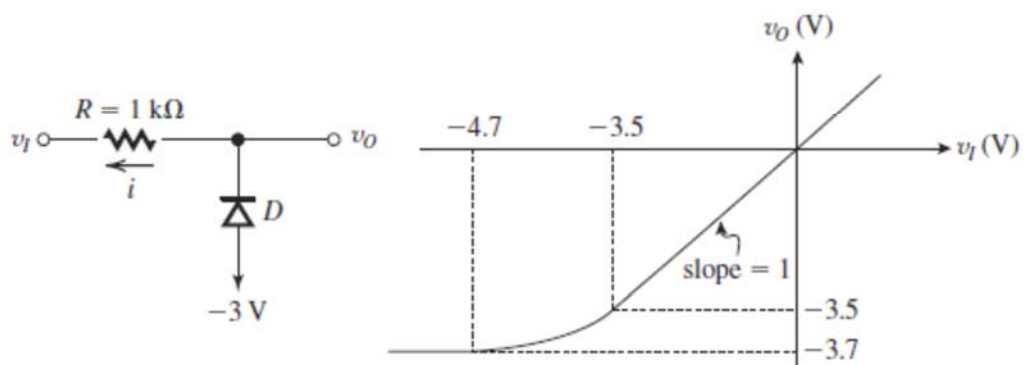

(d)

4.90

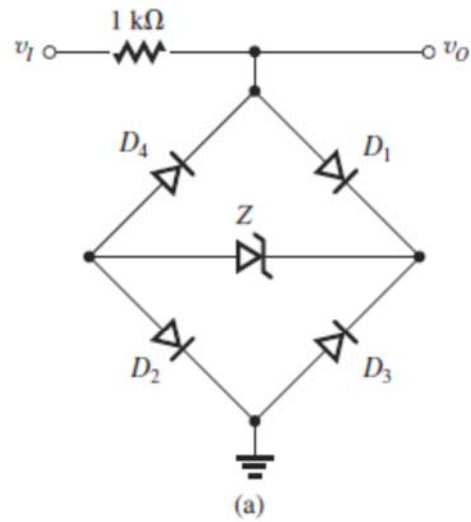

The limiter thresholds and the output saturation levels are found as $2 \times 0.7 + 6.8 = 8.2\text{ V}$. The transfer characteristic is given in Fig. (b). See figure on next page.

This figure belong to Problem 4.90, part b.

