

$$4.4 \quad a) 50 \text{ Hz} \rightarrow T(\text{period}) = 20 \text{ ms}$$

Two "blip" per period \rightarrow full wave rectification

$$b) \text{ Peak diode current} = 10 \text{ A} = C V_{\max} \cos \phi$$

$$\phi = \omega \delta = \frac{2\pi \times 50 \times 5 \times 10^{-3}}{0.5 \text{ ms}} = 0.157 \text{ rad} \\ = 9^\circ$$

$$V_{\max} = \frac{10}{10 \times 10^{-3} \times 2\pi \times 50 \times 0.157} = 20.4 \text{ V}$$

$$\text{But } \frac{v_{\text{unipole}}}{v_{\max}} = 1 - \cos \phi = 0.123$$

$$\rightarrow v_{\text{unipole}} = 0.25 \text{ V}$$

$$c) \text{ maximum load current} = \frac{v_{\max}}{R} = i_{\text{cm}}$$

$$\text{But } \frac{v_{\text{unipole}}}{v_{\max}} = \frac{T}{2\pi c}$$


$$\rightarrow R = \frac{1}{50 \times 2 \times 10^{-2} \times 0.123} \\ = 8.13 \Omega$$

$$\therefore N_{\text{cm}} = \frac{20.4}{8.13} = 2.5 \text{ A}$$

4.7

60 Hz

stepped down to
10 sin wt
(transformer)

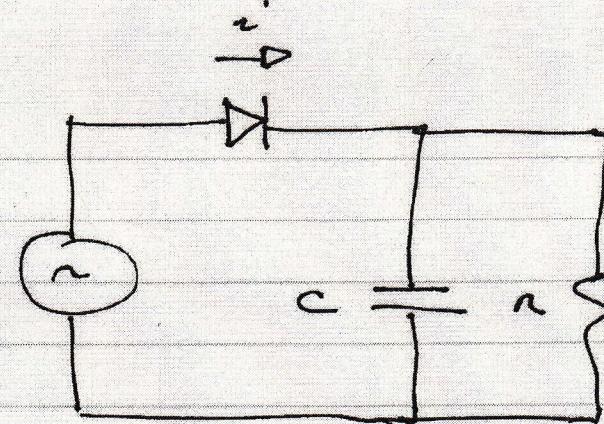

$$R = 100 \Omega$$

$$V_{max} = 100 \text{ mV} \times 0.1 \text{ K} = 10 \text{ V}$$

$$5 \text{ to } r_{\text{parallel}} = 0.5 \text{ V}$$

$$\frac{V_{\text{parallel}}}{V_{max}} = \frac{1}{20} = \frac{T}{2\pi C}$$

$$\rightarrow C = \frac{20}{60 \times 100} = 3.33 \text{ nF}$$

$$\cos \phi = 1 - \frac{V_{\text{parallel}}}{V_{max}} = 0.95$$

$$\phi = 18.2^\circ$$

$$i_{max} = C V_{max} \omega \sin \phi$$


$$= 3.33 \times 10^{-9} \times 20 \times 2\pi \times 60 \sin \phi$$

$$= 7.84 \text{ A}$$

Choose a 10-A diode rating.

220 kHz

4.20

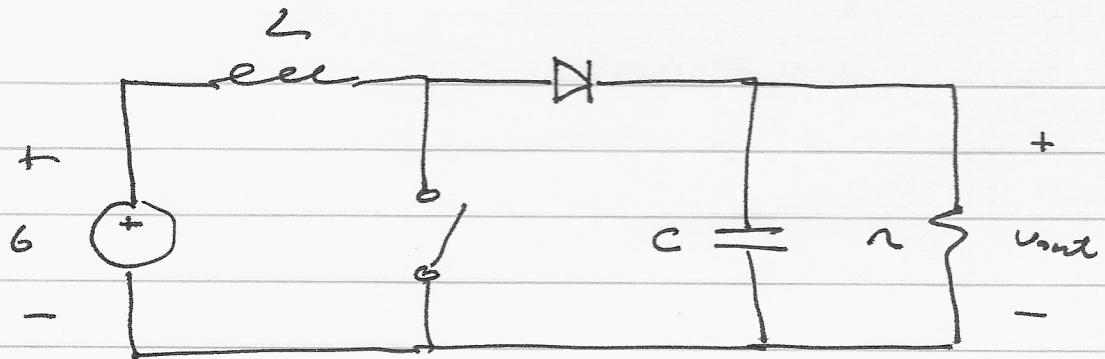

$$50 \text{ mA} @ 15V \rightarrow R = 300 \Omega$$

$$15 = \frac{6}{1-d} \rightarrow d = 0.6$$

$$L > \frac{6(0.4)(0.6)}{220 \times 10^3 \times 2 \times 0.05} = 66 \text{ mH}$$

\uparrow
dc load current

choose $L = 100 \text{ mH}$ (standard)

$$v_{\text{ripple}} = \left(\frac{V_0}{1-d} \right) \left(\frac{dt}{nc} \right) \leq 0.1 \text{ V}$$

$$C > \frac{15(0.6)}{220 \times 10^3 \times 0.1 \times 300} = 1.4 \mu\text{F}$$

choose $C = 2.2 \mu\text{F}$ (standard)

$$n_L = \frac{V_0}{R(1-d)^2} + \frac{V_0 dt}{2L}$$

$$n_{L,\text{pop}} = \frac{V_0 dt}{L} = \frac{6(0.6)}{10^{-4} \times 220 \times 10^3} = 0.16A$$



\uparrow
most flow through C

$$v_{\text{ripple}} \approx E_{\text{VR}} \times n_{L,\text{pop}} < 0.1 \text{ V}$$

$$\hookrightarrow E_{\text{VR}} < 0.62 \Omega$$

choose $E_{\text{VR}} \lesssim 0.2 - \Omega$ to be safe

4.23

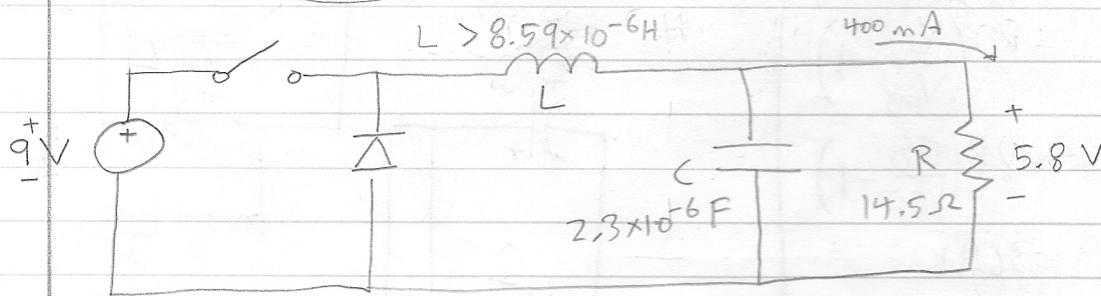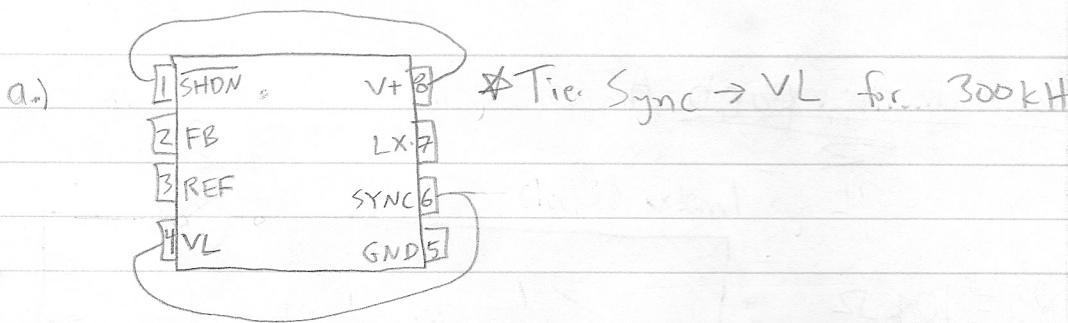

$$V_{out} = DV_o \quad 5.8 = 9(D) \quad D = 0.644 \quad T = 1/300k = 3.3 \mu s$$

$$L > \frac{V_o (1-D) DT}{2 \times \text{DC load current}} = \frac{9(1-0.644)(3.33 \times 10^{-6})}{2(0.4)} = 8.59 \times 10^{-6} \text{ H}$$

$$R = 5.8 / 0.400 = 14.5 \Omega$$

$$L > 8.59 \times 10^{-6} \text{ H}$$

$$i_{pp} = V_o (1-D) DT / L = 9(1-0.644) \cdot 0.644 (3.33 \times 10^{-6}) / 8.59 \times 10^{-6} = 0.799 \text{ A}$$

$$Z_c = R + \frac{1}{j\omega C} \quad |Z_c| = \sqrt{R^2 + \frac{1}{\omega^2 C^2}}$$

$$ESR = 0.08 \Omega = \frac{1}{\omega C} = \frac{1}{2\pi(300,000)C} = 6.62 \mu F$$

- closest we can get is 6.8 μF from Digikey.

$$|Z_c| = 0.08\sqrt{2} = 0.113 \Omega$$

$$\text{Vripple} = (i_{pp})(Z_c) = (0.113)(0.799) = 0.09 \text{ V rms}$$

$$i_{max} = \frac{DV_o}{R} + \frac{V_o (1-D) DT}{2L} = \frac{(0.644)9}{14.5} + \frac{9(1-0.644)(0.644)3.3 \times 10^{-6}}{2(8.59 \times 10^{-6})} = 0.796 \text{ amps}$$

$$i_{max} = 0.796 \text{ amps}$$

$$L = 8.6 \mu H$$

$$C = 6.62 \mu F$$

$$R = 14.5 \Omega$$



Circuit for part A:

$$R_2 = 10k\Omega$$


$$R_1 = R_2 \left(\frac{V_o}{V_{FB}} - 1 \right)$$

$$R_1 = 10k \left(\frac{5.0}{1.25} - 1 \right)$$


$$R_1 = 36.4k \\ \approx 36.5k$$

for 300 kHz,
 $L = 33 \mu H$

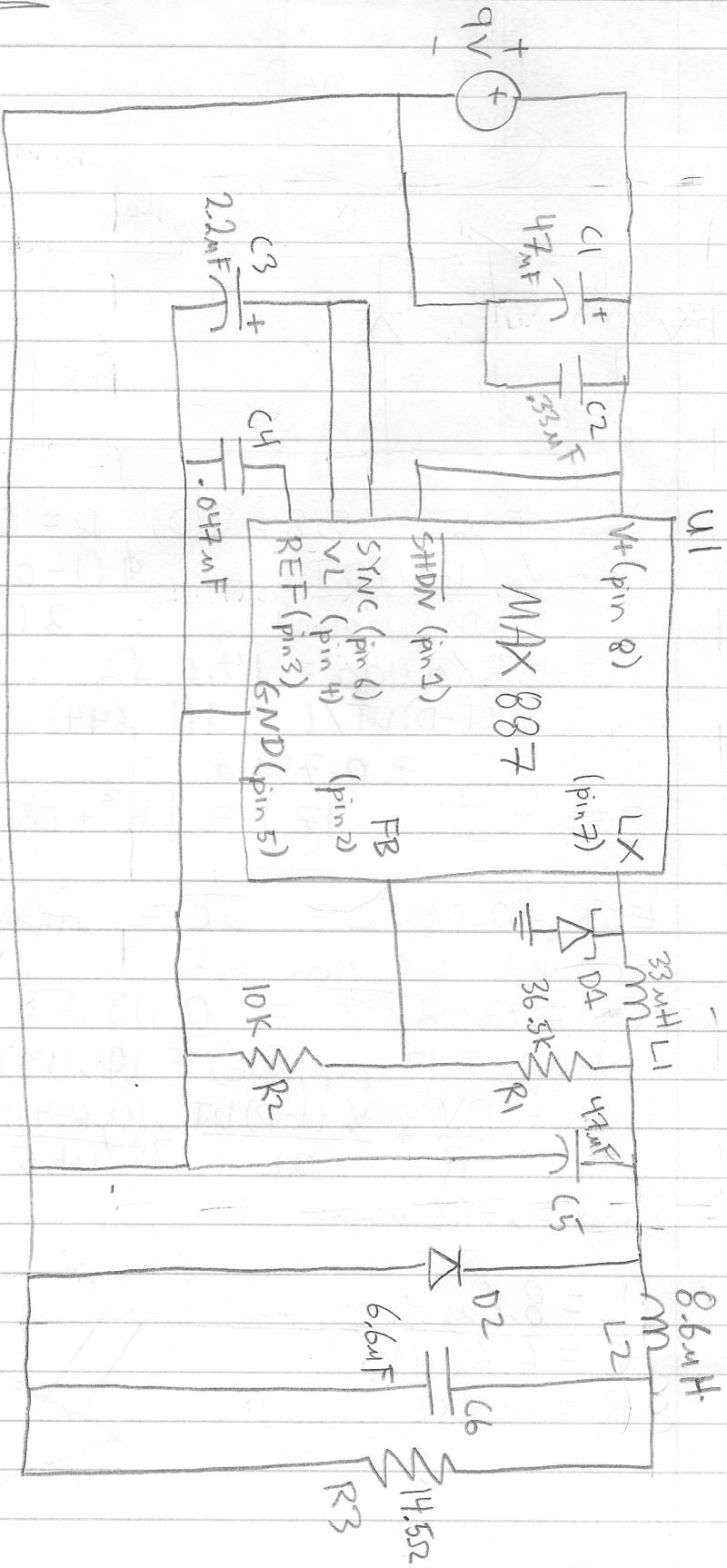* D1 is a
 1A Shottky
 Diode that
 prevents the
 slow internal
 diode of the
 N-channel MOSFET
 from turning on.



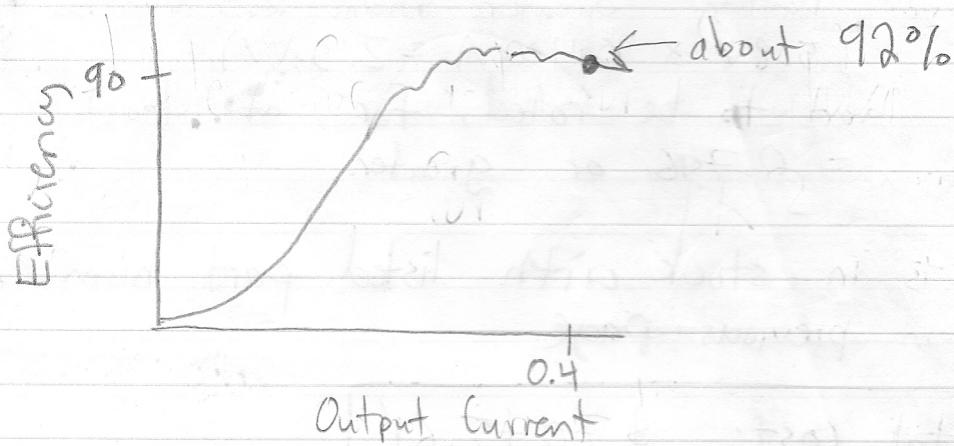b.) The operating efficiency of my design will be based on the efficiency of the MAX 887, which for our circuit looks like this.



The operating efficiency is about 92%

c.) Ordering Information from Digikey for 1000 of each part.
(continued on next page)

Part	Digikey #	Notes	Price for 1000
C1	2-1879291-2-ND	47μF, Aluminum, 16 V rated	\$265.73
C2	PCC1876TR-ND	0.33μF, Ceramic, 16 V rated	\$132.16
C3	PCE3169DKR-ND	2.2μF, Aluminum, 16 V rated	\$693.63
C4	PCC1729TR-ND	0.047μF, Ceramic, 16 V rated	\$63.42
C5	2-1879291-2-ND	47μF, Aluminum, 16 V rated	\$265.73
C6	PCE3171DKR-ND	6.8μF, Aluminum, 16 V rated	\$693.63
R1	P36.5KHDKR-ND	36.5K, Thick Film, 1W rated	\$4.16
R2	P10KGDKR-ND	10K, Thick Film, 1W rated	\$2.88
R3	SM6227FT14R7-ND	14.7Ω, Wirewound Surface Mount, 3W	\$761.26
L1	811-1138-2-ND	33μH, rated for 1A	\$494.00
L2	SRR6028-SR6YTR-ND	8.6μH, rated for 2.1 A	\$380.00
D1	568-4138-6-ND	Schottky, 1A fwd current, 60V reverse	\$122.20
D2	MA2YD2100LCT-ND	Rectifier, 1A fwd, 15V DC reverse	\$166.91
V1	MAX887HEAT-ND	MAX887 switching DC-DC converter	\$3000.00


- For C6, we chose a part with an ESR that fit with our part A calculations.
- For R3, we need a resistor with a power rating greater than 2.3 Watts.
 $(5.8V \times 0.400A = 2.3W)$
- L2 had to be rated for at least $i_{Lmax} = 0.796$ or greater.

* Parts in stock with listed part numbers from previous page

- Total cost: \$7045.61
for 1000 of each part.

4.29

a)

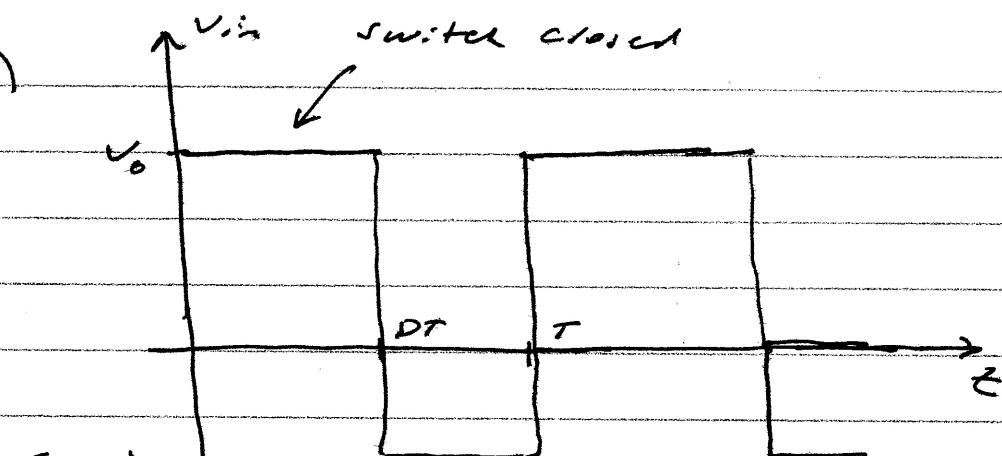

$$\langle V_{out} \rangle = \frac{V_0}{T} \cdot \tau$$

$$\frac{\tau}{T}$$

switch open, $i_L = 0$ negativezero diode voltage if $i_L > 0$

Prove shortly

$$b) \langle V_L \rangle = \langle V_{in} \rangle = 0$$

$$0 = \frac{1}{T} [V_0 DT + \langle V_{out} \rangle (1-D)T]$$

$$\rightarrow V_{out} = \frac{-DV_0}{1-D}$$

c) switch closed

$$C \frac{di_L}{dt} = V_0$$

$$i_L(\text{max})$$

$$i_L(\text{min})$$

$$i_L(\text{max}) - i_L(\text{min}) = \frac{V_0 DT}{2}$$

4.29 (cont) Inductor energy stored = $\frac{1}{2} L i_L^2 - \frac{1}{2} L i_{L\text{avg}}^2$

$$= \frac{1}{2} \left[\frac{-DV_0}{1-D} \right]^2 DT$$

Load Power $\frac{V_0 DT}{2}$

charge time
switch off time

$$\left(\frac{1}{2} L \right) (i_{L\text{max}} - i_{L\text{min}}) (i_{L\text{max}} + i_{L\text{min}})$$

$$= \frac{DT}{2} \frac{D^2 V_0^2}{(1-D)^2}$$

→ $i_{L\text{max}} + i_{L\text{min}} = \frac{2V_0 D^2}{n(1-D)^2}$


$$i_{L\text{max}} - i_{L\text{min}} = \frac{V_0 DT}{2}$$

$$i_{L\text{max}} = \frac{V_0 D^2}{n(1-D)^2} \pm \frac{V_0 DT}{2L}$$

d) $i_{L\text{max}} > 0$


$$\rightarrow L > \frac{nT (1-D)^2}{2D} = \frac{R}{2} DT \left(\frac{V_0}{V_{\text{max}}} \right)^2$$

e) $nC \gg T$

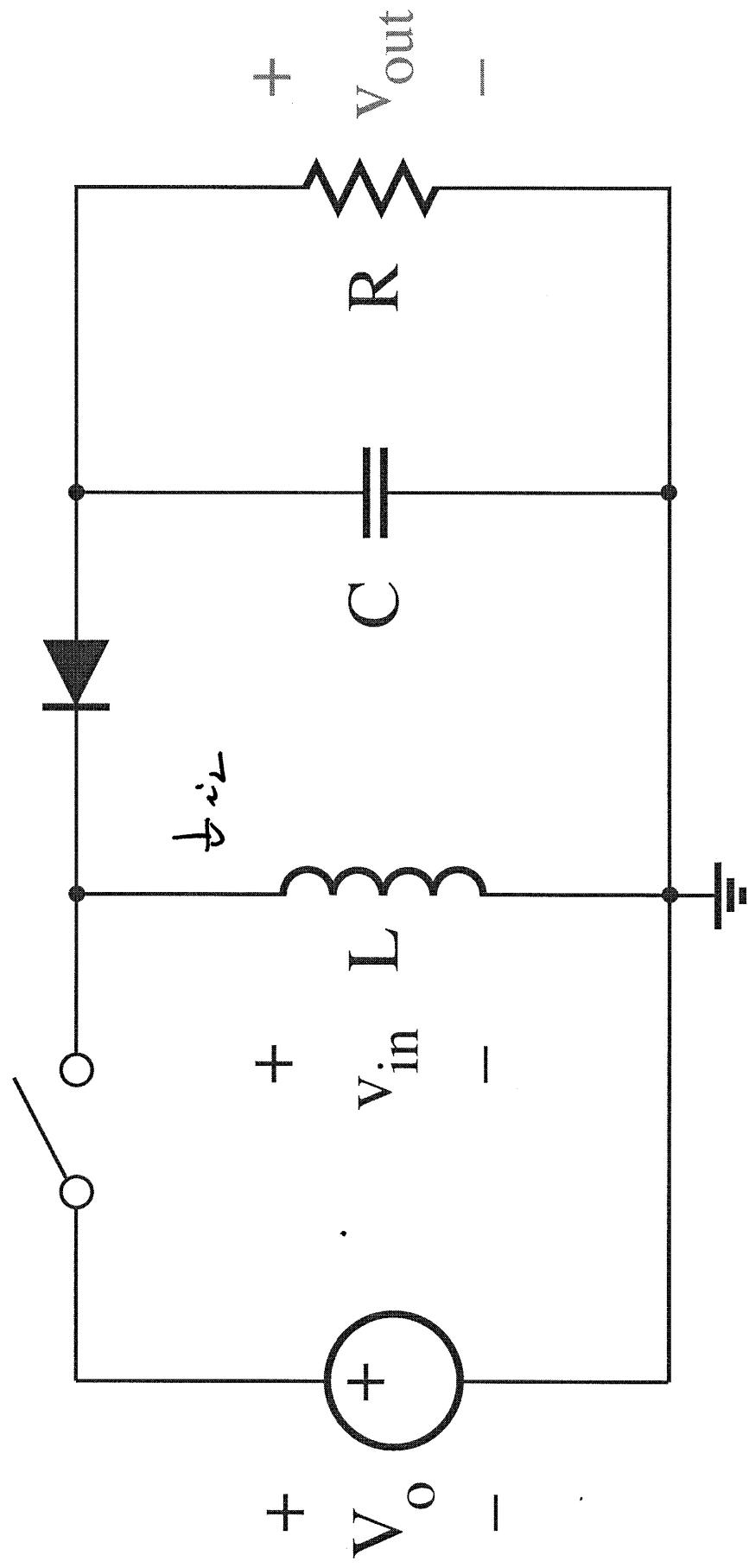

4.29

4.41

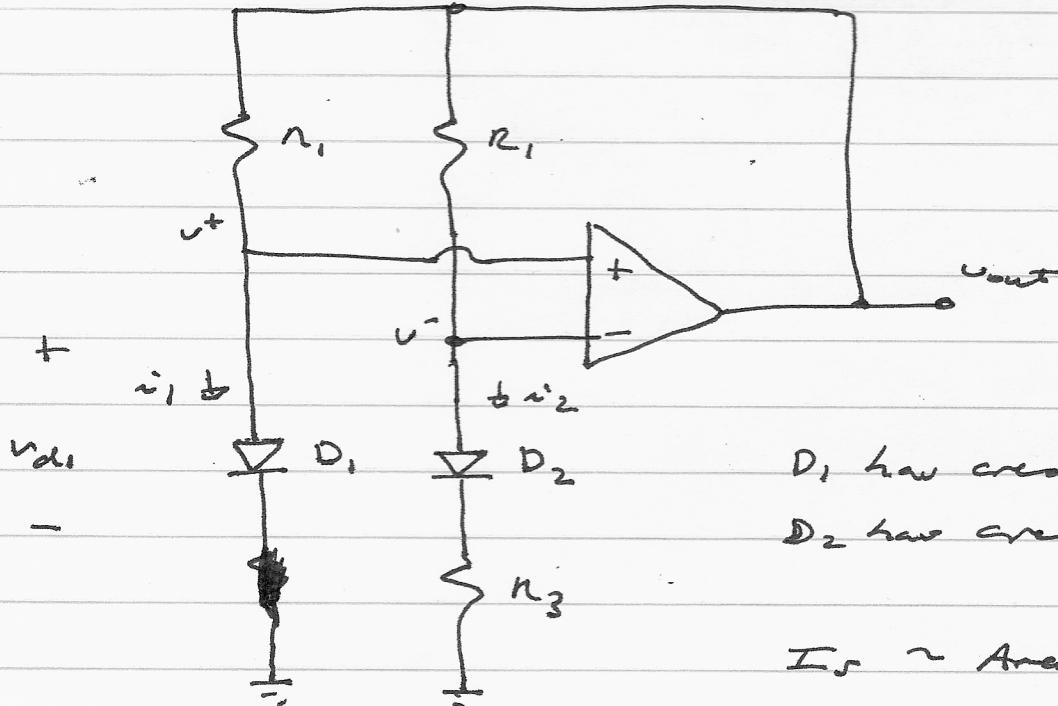

$$v^+ = v^- \rightarrow i_1 = i_2$$

$$\frac{kT}{2} \ln\left(\frac{i_1}{XA I_{sr}'}\right) = \frac{kT}{2} \ln\left(\frac{i_2}{A I_{sr}'}\right) + i_2 R_3$$

$$i_2 = \frac{1}{R_3} \left(\frac{kT}{2} \right) \ln\left(\frac{1}{X}\right) \quad \text{PTAT current}$$

$$= i_1$$

$$v_{out} = v_{de1} + \left(\frac{n_1}{n_3} \right) \left(\frac{kT}{2} \right) \ln\left(\frac{1}{X}\right)$$

This has the form needed to cancel out the linear dependence on temperature

At $T \uparrow$ $v_{de1} \downarrow$

so $\ln\left(\frac{1}{X}\right) > 0$ is required

$$\xrightarrow{\hspace{1cm}} \underline{X < 1}$$