


7. 37

$$K' \frac{w}{L} = 1.6 \text{ mA/V}^2$$

$$v_T = 0.6 \text{ V}$$

$$v_g = \frac{10}{10+47} (12) = 2.1 \text{ V} \quad \left\{ v_{sr} = 2.1 - 1.2 \text{ mA} \right.$$

$$v_s = 1.2 \text{ Vd}$$

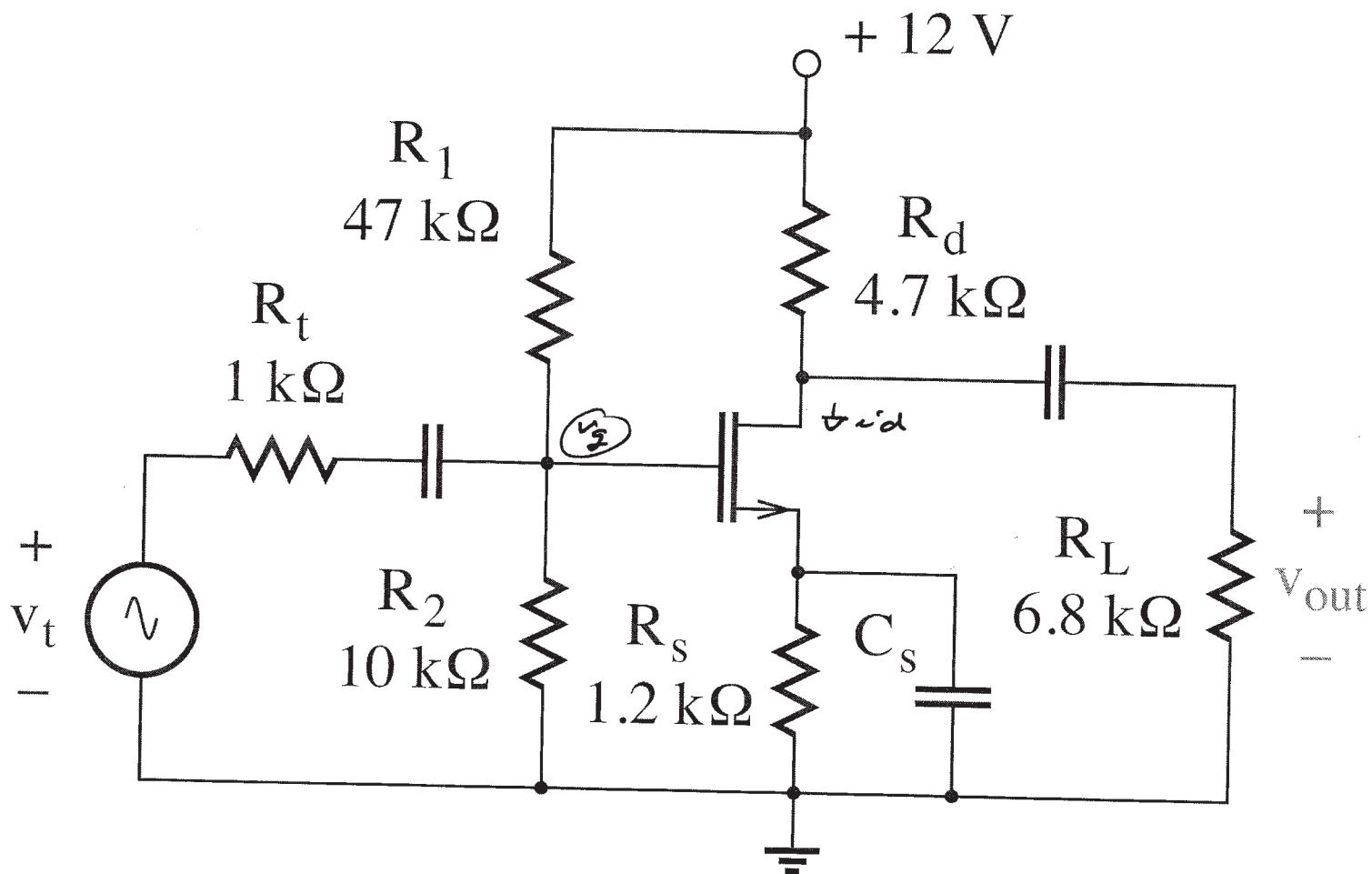

$$v_{sr} = 2.1 - 1.2 \left(\frac{1}{2}\right)(1.6)(v_{sr} - 0.6)^2$$

$$0.96 v_{sr}^2 + 0.15 v_{sr} - 1.7v = 0$$

$$\rightarrow v_{sr} = 1.42, -2.7$$

$$i_{d1Q} = \frac{1}{2}(1.6)(1.42 - 0.6)^2 = 0.551 \text{ mA}$$

7.37 (continued)

$$g_m = \sqrt{2 \times 1.6 \text{ mA/V}^2 \times 0.55 \text{ mA}} = 1.26 \times 10^{-3} \text{ V}$$

Common source amplifier: $A_{vm} = -g_m r_{dl}'$

$$r_{dl}' = 4.7k \parallel 16.8k = 2.78k$$

$$A_{vm} = -1.26 \times 10^{-3} \text{ V} \times 2.78 \times 10^3 \text{ S} = -3.50$$

$$r_{in} = 47k \parallel 10k = 8.25k$$



$$\text{Loading factor} = \frac{r_{in}}{r_{in} + r_{out}} = \frac{8.25k}{8.25k + 1k} = 0.892$$

$$A_{vm}^{TOTAL} = -3.50 \times 0.892 = \underline{-3.1}$$

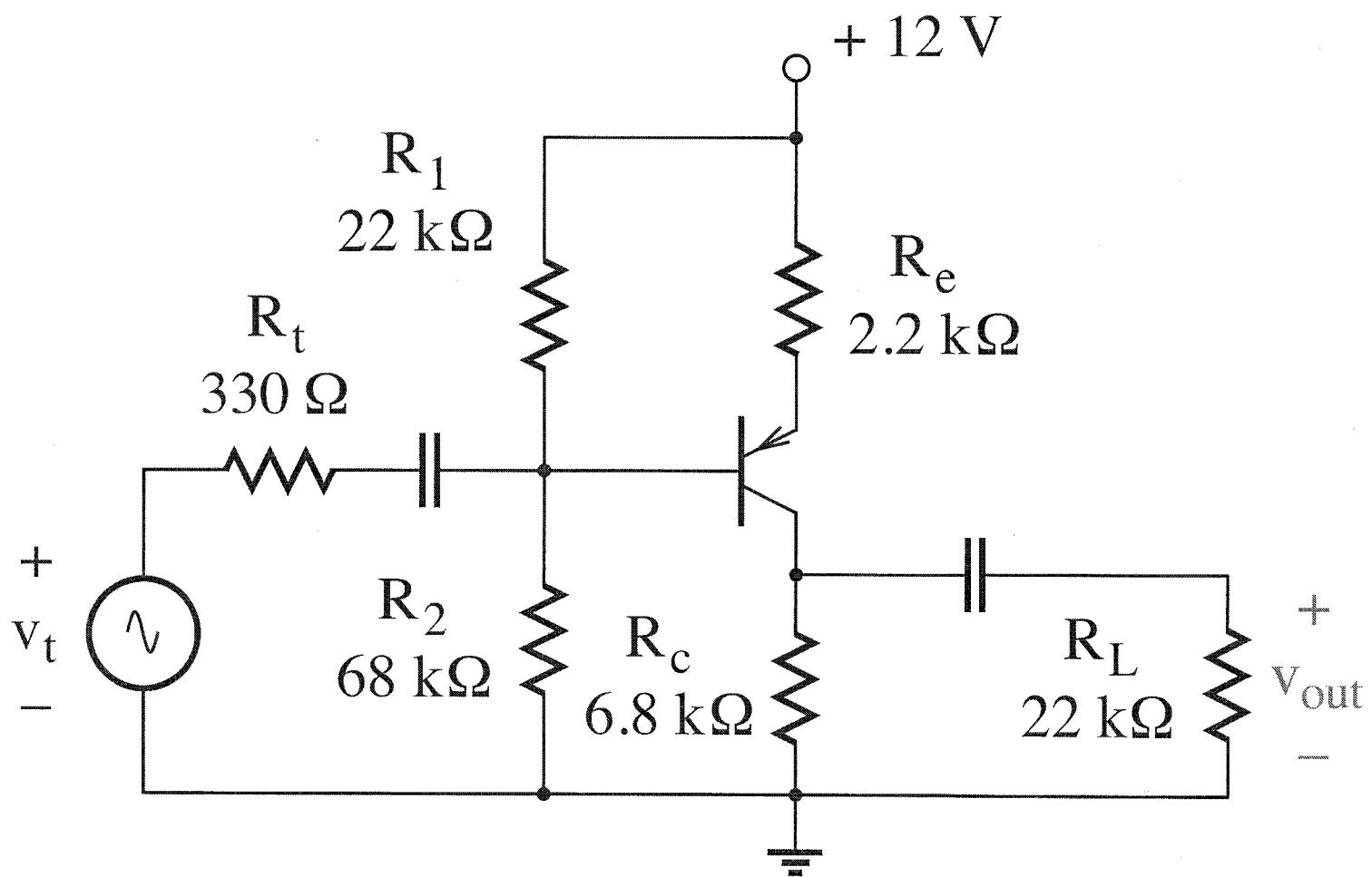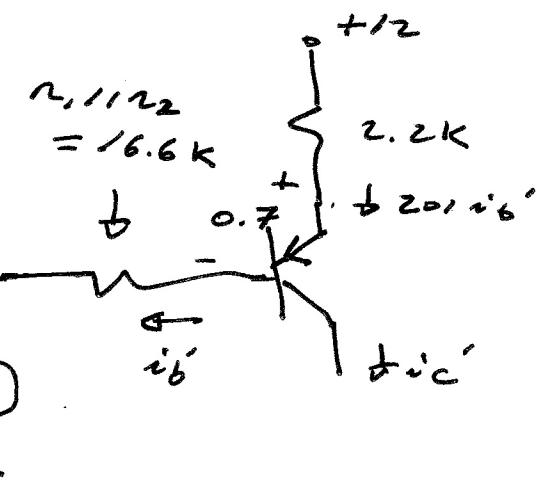7. 41

$$\beta_{\text{f}} = \beta_0 = 200$$

$$12 \left(\frac{68}{68+22} \right) = 9.07$$



$$12 = 9.07 + 16.6 i_b' + 0.7 + 200 i_b' (200)$$

$$\rightarrow i_b' = \frac{2.23}{459} \quad i_c' = -i_b' = \frac{2.23 (200)}{459}$$

$$i_m = \frac{|i_c|_{\text{Q1}}}{kT_B} = \frac{0.972 \text{ mA}}{25.9 \text{ mV}} = 37.5 \times 10^{-3} \text{ A} = 0.972 \text{ mA}$$

$$r_{\pi} = \frac{R_o}{S_m} = 5.77 \text{ k}\Omega$$

(7.41) common emitter amplifier (no bypass)
 $\omega = 6.8K / 122K = 5.18K$

$$A_{vm} = \frac{-g_m r_e'}{1 + g_m r_e' (1 + \frac{1}{g_o})}$$

$$= \frac{-37.5 \times 10^{-3} \times 5.18 \times 10^3}{1 + 37.5 \times 10^{-3} \times 2.2 \times 10^3 \times 1.005}$$

$$= -2.32$$

$$r_{in} = \underbrace{r_1 / r_2}_{16.6K} / \left[r_T + \underbrace{(1 + g_o) r_e'}_{447.5K} \right]$$

$$= 16K$$


$$\text{Loading factor} = \frac{16K}{16K + 0.33K} = 0.980$$

$$A_{vm}^{\text{TOTAL}} = -2.32 \times 0.980 = -2.27$$

$$7.46 \quad K' \frac{w}{L} = 3.6 \text{ mA/V}^2 \quad v_T = -0.5V$$

$$-id = \frac{1}{2}(3.6)(v_{sr} - v_T)^2$$
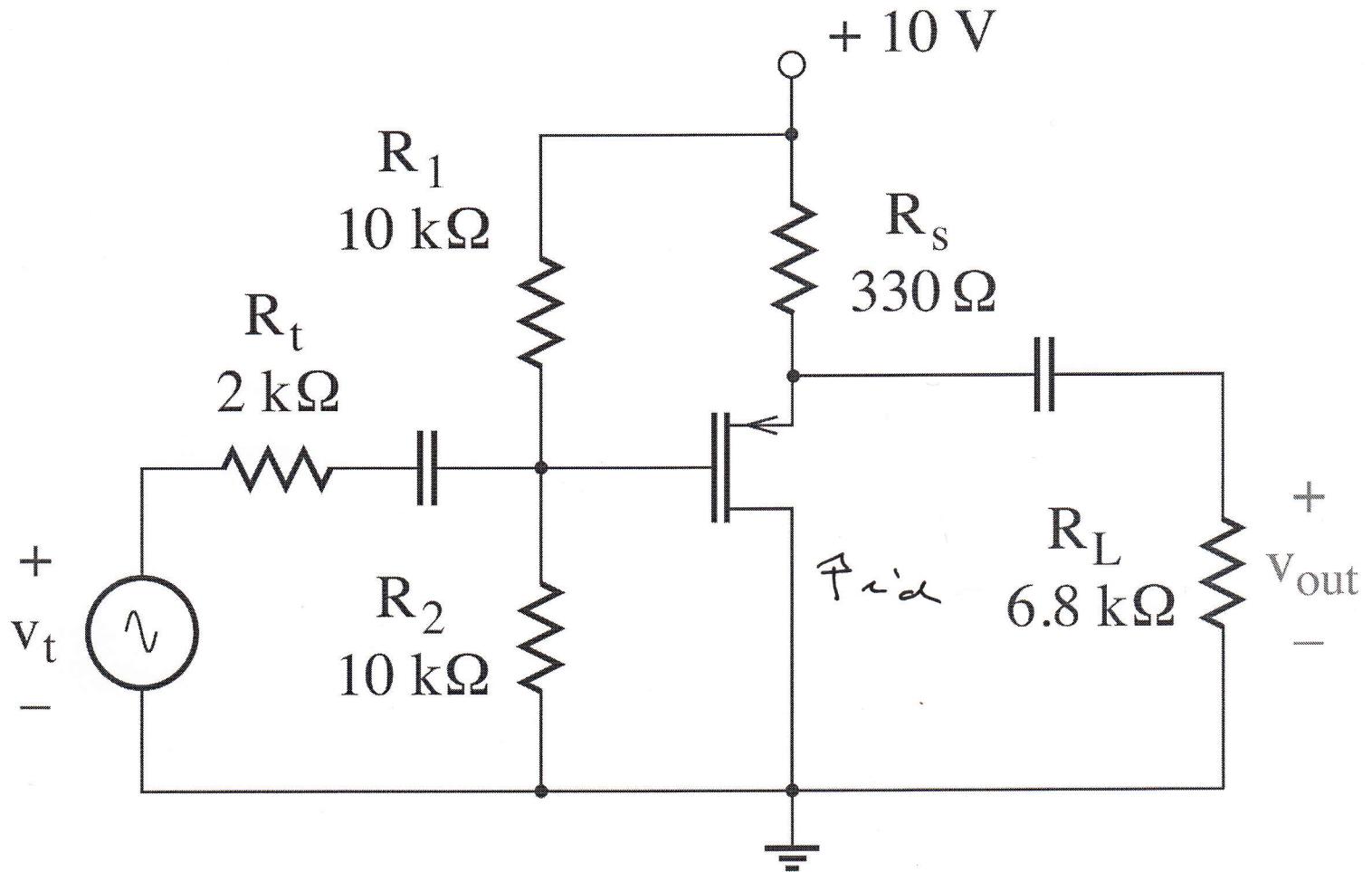
$$\begin{aligned} v_S &= 10 \left(\frac{10}{10+10} \right) = 5 \\ v_T &= 10 + 0.33 id \end{aligned} \quad \left\{ \begin{array}{l} v_{sr} = -5 - 0.33 id \\ \end{array} \right.$$



$$v_{sr} = -5 + 0.6(v_{sr} + 0.5)^2$$

$$0.6 v_{sr}^2 - 0.4 v_{sr} - 4.85 = 0 \rightarrow v_{sr} = -2.53, 3.2 \quad \cancel{\text{X}}$$

$$id|_a = -1.8(-2.53 + 0.5)^2 = -7.41 \text{ mA}$$

$$g_m = \sqrt{2K' \frac{w}{L} |i_{d(a)}|} = 7.3 \times 10^{-3} \text{ V}$$

7.46

common drain

cont.

$$A_{vn} = \frac{g_m n'}{1 + g_m n'}$$

$$n' = 0.33K // 6.8K = 0.315K$$

$$g_m n' = 2.2$$

$$\rightarrow A_{vn} = 0.647$$


$$LF = \frac{r_o}{r_{in} + 2K}$$

$$r_{in} = 10K // 10K = 5K$$

$$\rightarrow LF = 0.714$$

$$A_{vn}^{\text{total}} = A_{vn} \times LF = \underline{0.5}$$
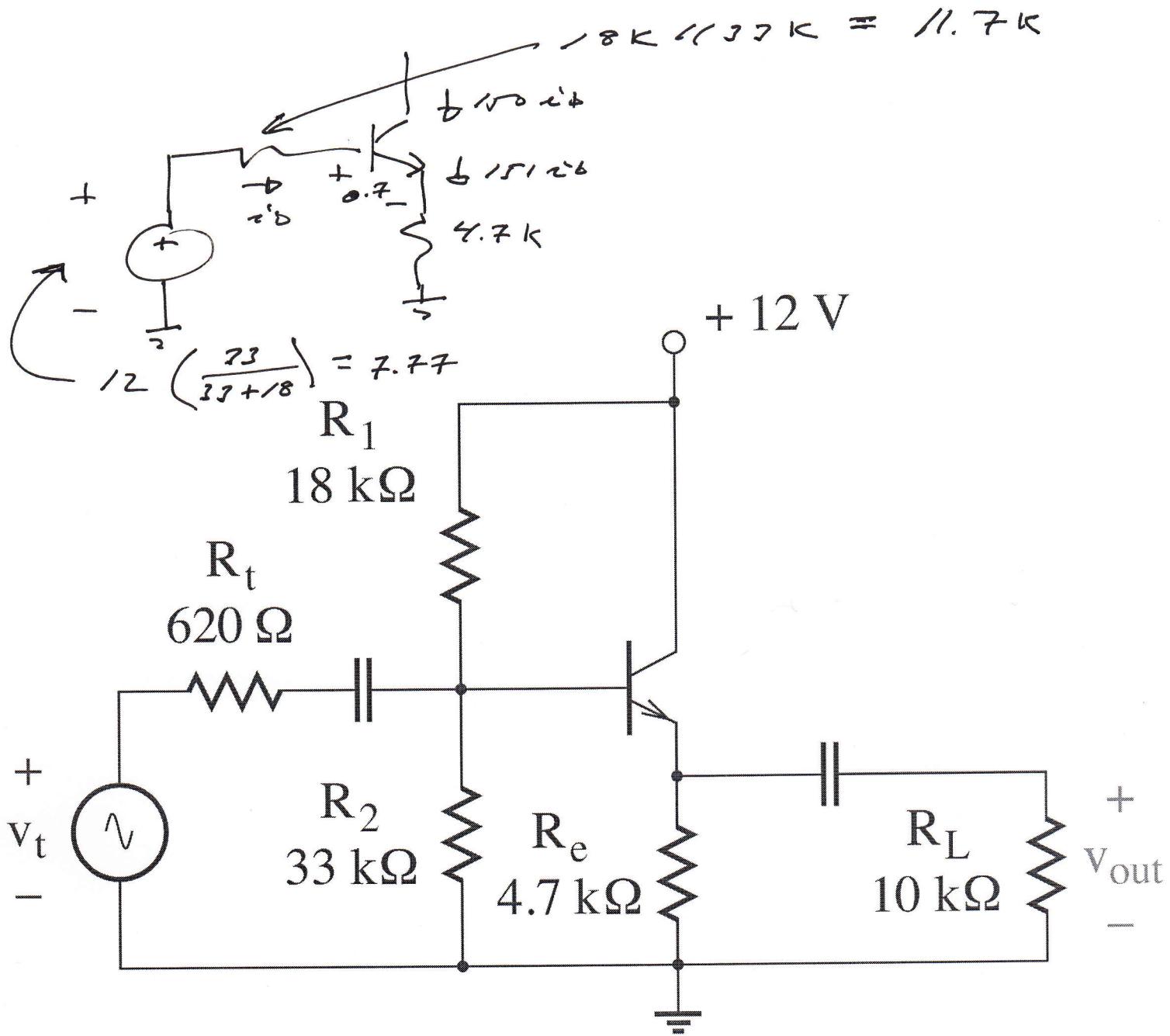
$$R_{\text{in}} = \beta_F = \beta_0 = 150$$



$$7.77 = 11.7 \text{ mA} + 0.7 + 151 \text{ mA} (4.7)$$

$$\text{~.6} = \frac{7.07}{721} \quad \text{~.1mA} = 150 \left(\frac{7.07}{721} \right) = 1.47 \text{ mA}$$

$$S_m = \frac{1.47 \text{ mA}}{25.9 \text{ mV}} = 56.8 \times 10^{-3} \text{ V}$$

$$r_T = \frac{\beta_0}{S_m} = 2.64 \text{ k}\Omega$$

7.49
(cont.)

Common collector

$$A_{m'} = \frac{g_m r_e' (1 + \frac{1}{R_o})}{s_m r_e' (1 + \frac{1}{R_o})}$$

$$r_e' = 4.7K // 10K = 3.2K$$

$$s_m r_e' (1 + \frac{1}{R_o}) = 183$$

$$A_m = 0.995$$

$$\begin{aligned} r_m &= r_1 // r_2 // [r_o + \underbrace{(1 + R_o) r_e'}_{48.7K}] \\ &= 11.4K \end{aligned}$$

$$LF = \frac{r_m}{r_m + 0.62K} = 0.848$$

$$A_m^{\text{TOTAL}} = A_m \times LF = \underline{0.84}$$

$$\rightarrow \text{current gain } A_{in} = A_m \frac{r_m}{r_L}$$

$$A_{in} = 0.995 \frac{11.4K}{10K} = 1.13$$

7.60

$$\text{stage 2} \quad g_{m2} = \frac{1.2 \text{ mA}}{25.9 \text{ mV}} = 46.3 \times 10^{-3} \text{ V}$$

$$r_{\pi 2} = \frac{R_o}{g_{m2}} = 2.16 \text{ k}\Omega$$

$$A_{vm}^{(2)} = \frac{-g_{m2} r_{ci}}{1 + g_{m2} r_{ci} (1 + \frac{1}{g_o})}$$

$$= \frac{-46.3 \times 10^{-3} \text{ V} \times 5 \text{ k} \times 10^3 \Omega}{1 + 46.3 \times 10^{-3} \text{ V} \times 1 \times 10^3 \Omega (1.01)}$$


$$= -4.85$$

$$r_{in}^{(2)} = \underbrace{[r_{\pi 2} + (1 + g_o) 1 \text{ k}\Omega]}_{+20 \text{ V} / 103.2 \text{ k}\Omega} \parallel (r_3 \parallel r_4) = 8.12 \text{ k}\Omega$$

$$R_1 \parallel R_2 = 10 \text{ k}\Omega$$

$$R_3 \parallel R_4 = 10 \text{ k}\Omega$$

$$\beta_F = R_o = 100$$

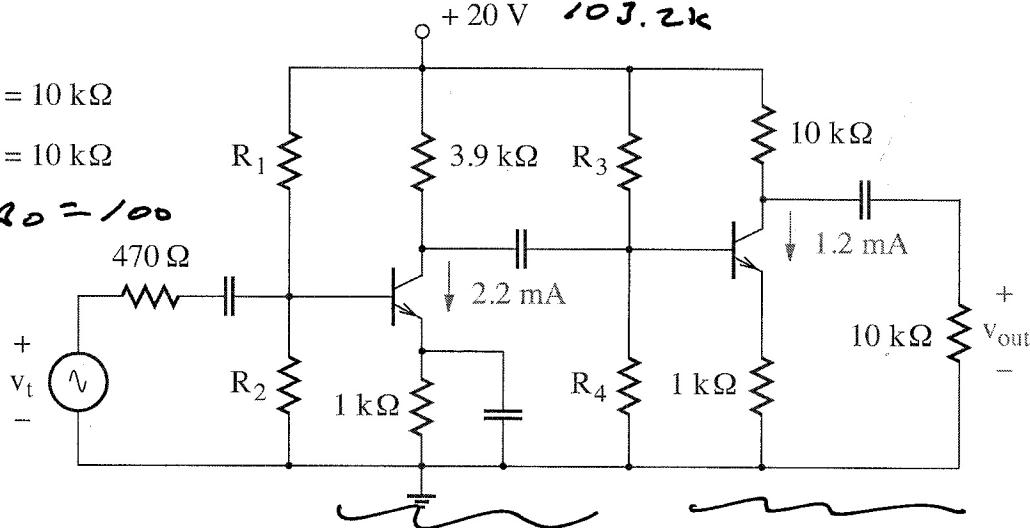stage 1
CEstage 2
CE (no bypass)

$$\text{stage 1} \quad g_{m1} = \frac{2.2 \text{ mA}}{25.9 \text{ mV}} = 84.9 \times 10^{-3} \text{ V}$$

$$r_{\pi 1} = \frac{R_o}{g_{m1}} = 1.18 \text{ k}\Omega$$

$$A_{vm}^{(1)} = -g_{m1} r_{ci} \xrightarrow{r_{in}^{(2)} \parallel 3.9 \text{ k}\Omega} = -232$$

$$r_{in}^{(1)} = r_1 \parallel r_2 \parallel r_{\pi 1} = 1.05 \text{ k}\Omega$$

$$\text{loading factor} = \frac{1.05}{1.05 + 0.87} = 0.691$$

$$A_{vm}^{\text{TOTAL}} = 0.691 \times (-232) \times (-4.85) = \underline{\underline{778}}$$

7.62

$$K' \frac{w}{L} = 2.2 \text{ mA/V}^2$$

$$g_m = \sqrt{2 \omega_{ul} K' \frac{w}{L}} = 2.10 \times 10^{-3} \text{ A}$$


$$\infty = \infty$$

$$B_0 = 120$$

$$g_m z = \frac{n_{cl} q}{kT/2} = \frac{0.1 \text{ mA}}{25.8 \text{ mV}} = 3.86 \times 10^{-3} \text{ A}$$

$$R_1 \parallel R_2 = 60 \text{ k}\Omega$$
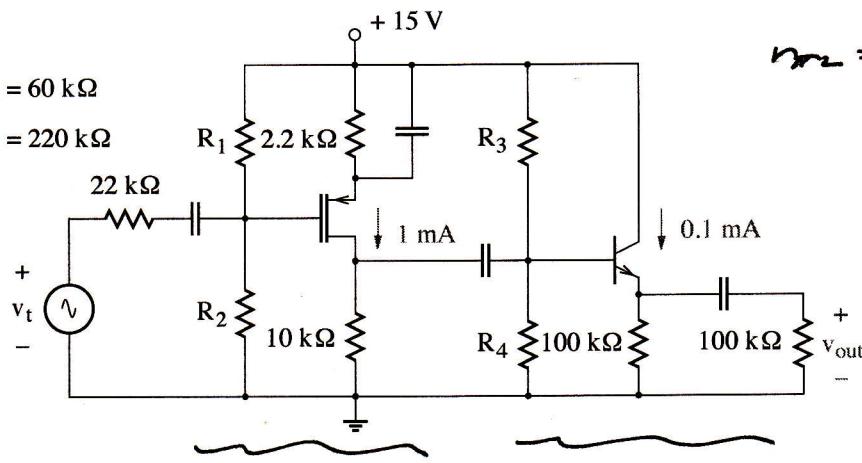
$$R_3 \parallel R_4 = 220 \text{ k}\Omega$$



$$r_{mz} = \frac{B_0}{g_m} = 31.1 \text{ k}\Omega$$

stage 1 stage 2

CS ~~100k // 100k~~ CC

$$A_{v_m}^{(2)} = -\frac{g_m r_{e2}' (1 + \frac{1}{B_0})}{g_m r_{e2}' (1 + \frac{1}{B_0}) + 1} = \frac{195}{195 + 1} = 0.995$$

$$r_{in}^{(2)} = r_2 \parallel r_4 \parallel [r_2 + (B_0 + 1)r_{e2}'] = \cancel{\underline{\underline{6.08 \text{ M}\Omega}}} \cancel{\underline{\underline{50 \text{ k}\Omega}}} 212 \text{ k}\Omega$$

$$A_{v_m}^{(1)} = -g_m r_{e1}' = \cancel{\underline{\underline{-20.0}}} \text{ }$$

$$\cancel{\underline{\underline{10 \text{ k}\Omega // r_{in}^{(2)}}}} = \cancel{\underline{\underline{9.55 \text{ k}\Omega}}}$$

$$r_{in}^{(1)} = r_1 \parallel r_2 = 60 \text{ k}\Omega$$

$$LF = \frac{r_{in}^{(1)}}{r_{in}^{(1)} + r_L} = \frac{60}{60 + 22} = 0.772$$

$$A_{v_m}^{total} = (LF \times A_{v_m}^{(1)} \times A_{v_m}^{(2)}) = \cancel{\underline{\underline{-15}}} - 15$$