
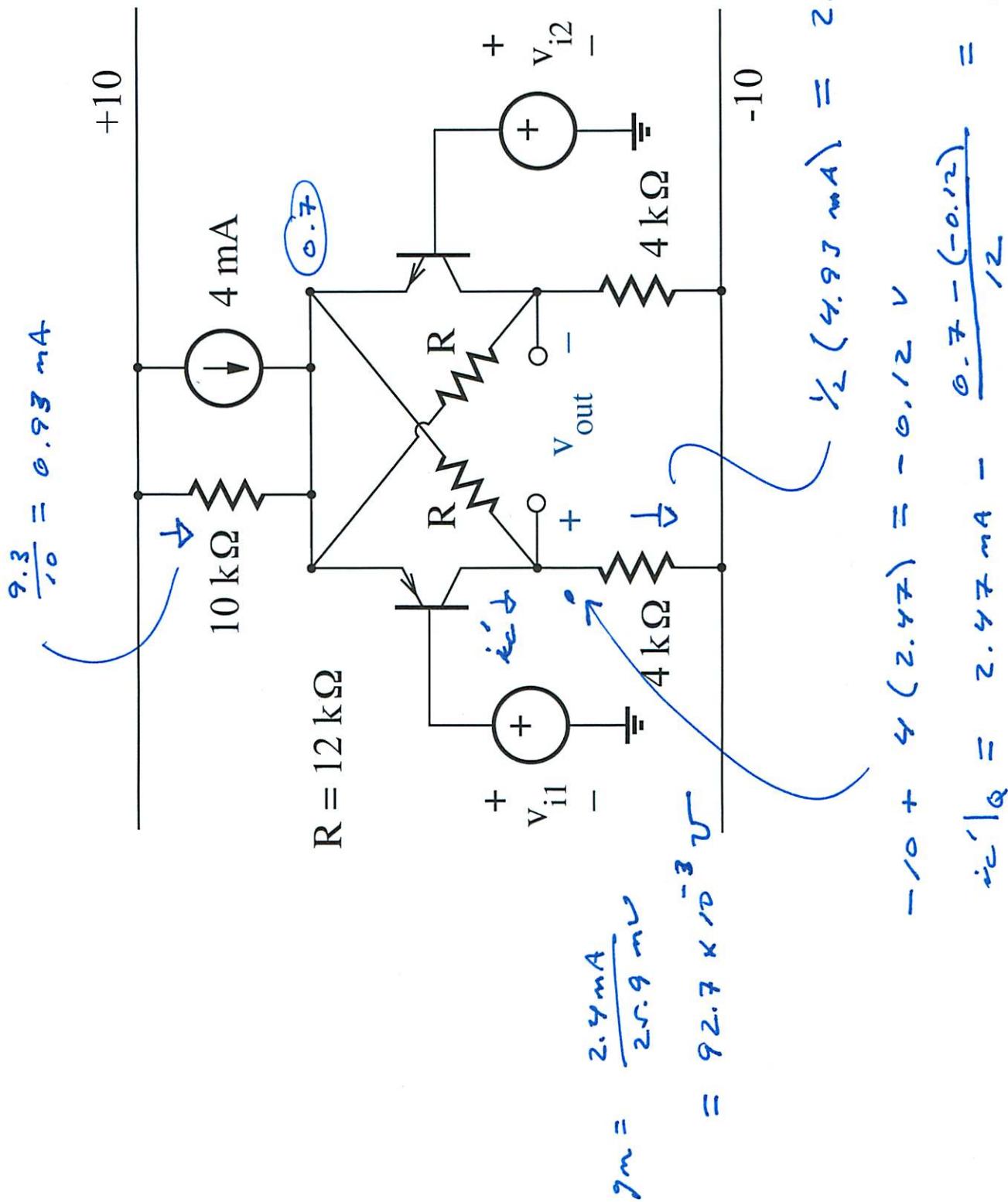


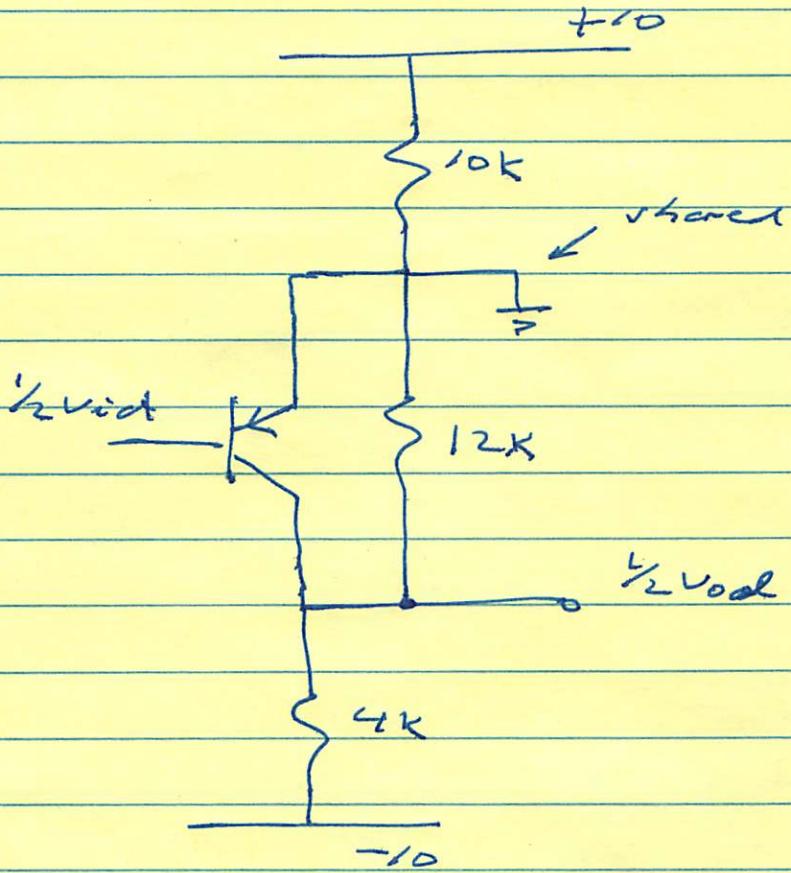9.4

Biasing calculation for $V_{i1} = V_{i2} = 0$



ac
differential mode^ half circuit




$$\frac{\frac{1}{2}V_{\text{odd}}}{\frac{1}{2}V_{\text{odd}}} = A_{\text{odd}} = -g_m \underbrace{(12\text{K}/4\text{K})}_{8\text{K}}$$


$$A_{\text{odd}} = -92.7 \times 10^{-3} \text{ m} \times 3 \times 10^3 \text{ S} = -278$$

ac

Common mode half circuit

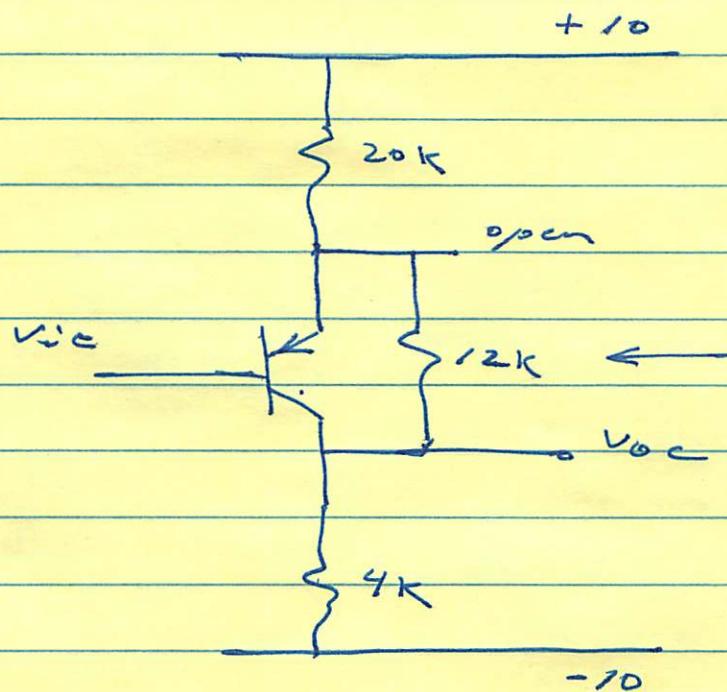

Small-signal circuit

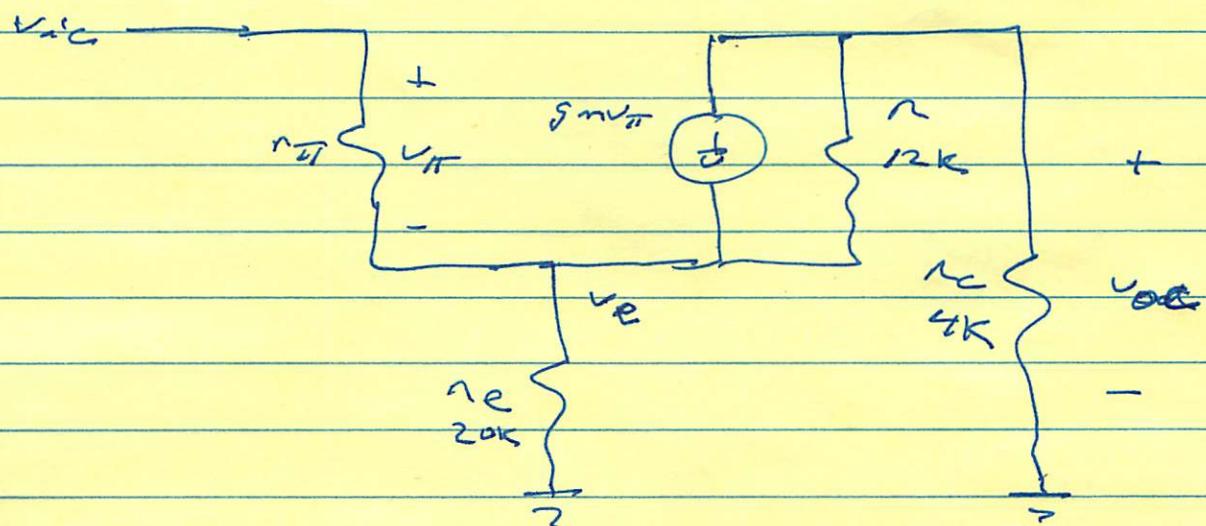

$$R_H = \frac{R_O}{g_m} = \frac{100}{g_m} = 1.08 \text{ k}$$

$$j\pi(v_{ic} - v_e) + g_m(v_{ic} - v_e) + G(v_{oc} - v_e) \xrightarrow{\frac{1}{R}} \\ = Gev_e$$

$$g_m(v_{oc} - v_e) + G(v_{oc} - v_e) + G_c v_{oc} = 0$$

$$\begin{pmatrix} Ge + s_m + s\pi + G & -G \\ -s_m - G & G + G_c \end{pmatrix} \begin{pmatrix} v_e \\ v_{oc} \end{pmatrix} = \begin{pmatrix} s_m + s\pi \\ -s_m \end{pmatrix}$$

$$v_{oc} = v_{ic} - \frac{\det \begin{pmatrix} Ge + s_m + s\pi + G & s_m + s\pi \\ -s_m - G & -g_m \end{pmatrix}}{\det \begin{pmatrix} Ge + s_m + s\pi + G & -G \\ -s_m - G & G + G_c \end{pmatrix}}$$

$$\frac{v_{oc}}{v_{ic}} = A_{ce} = \frac{-s_m Ge + G s\pi}{G e G + s\pi G + G_c G e + G_c s_m + G_c s\pi + G_{ce} G}$$

$$= \frac{-R_o R_{nc} + \cancel{R_{en} R_{nc}}}{r_\pi R_{nc} + R_{nc} + r_\pi r_n + R_o R_{en} + R_{en} + R_{nc}}$$


$$= \frac{-R_o R_{nc} + \frac{R_{en}}{R}}{R_o + (1+R_o)R_e + \frac{r_\pi R_{nc} + R_{en} + R_{nc}}{R}}$$

This reduces to the proper form as $n \rightarrow \infty$

$$A_{CC} = - \frac{400K - \frac{10K}{3}}{1.08K + 1010K + \frac{1.08K}{3} + 2.5K + \frac{5}{6}(1.08K)}$$
$$= -0.391$$

right!


9.5

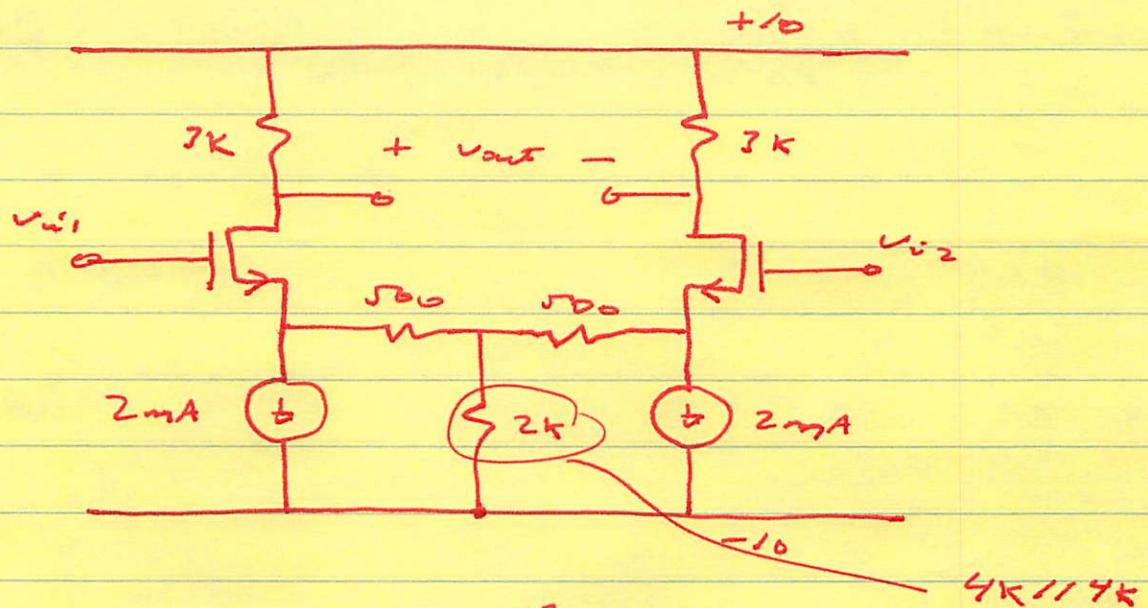

$$s_{m1} = g_{m2} = 5 \times 10^{-3} \text{ V}$$


$4k\Omega // 4k\Omega$

Half circuit for Add

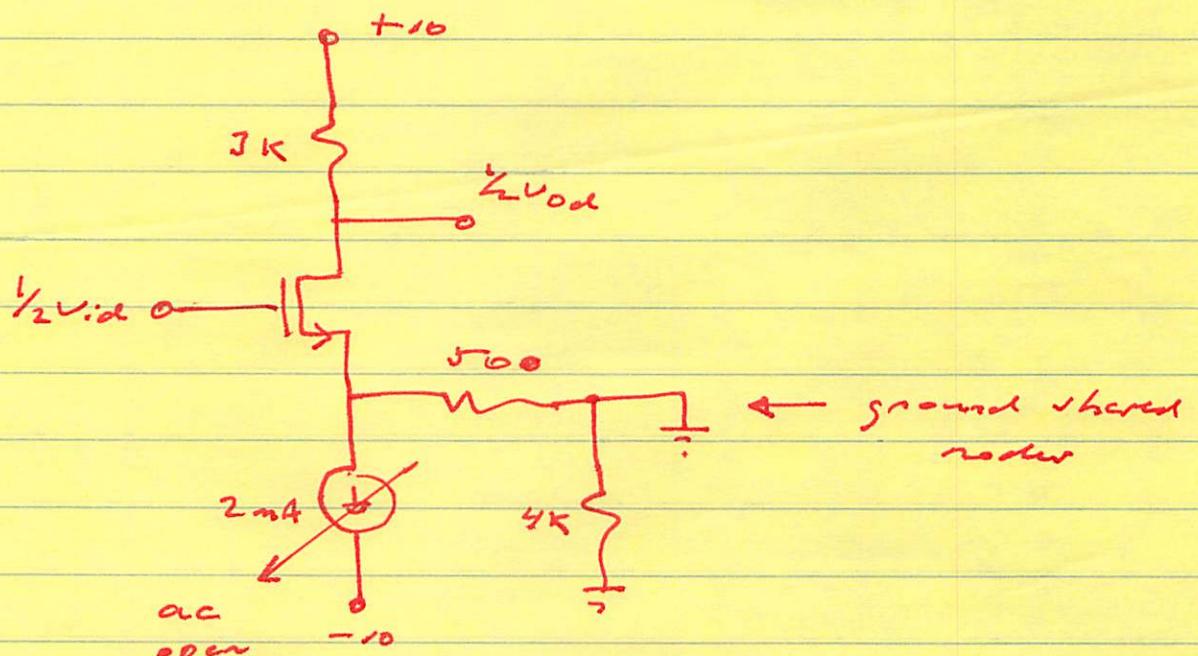


$$A_{dd} = \frac{\frac{1}{2}v_{uid}}{\frac{1}{2}v_{uid}} = \frac{-g_m(3k)}{1 + g_m(0.5k)} = -4.29$$

Half circuit for Acc

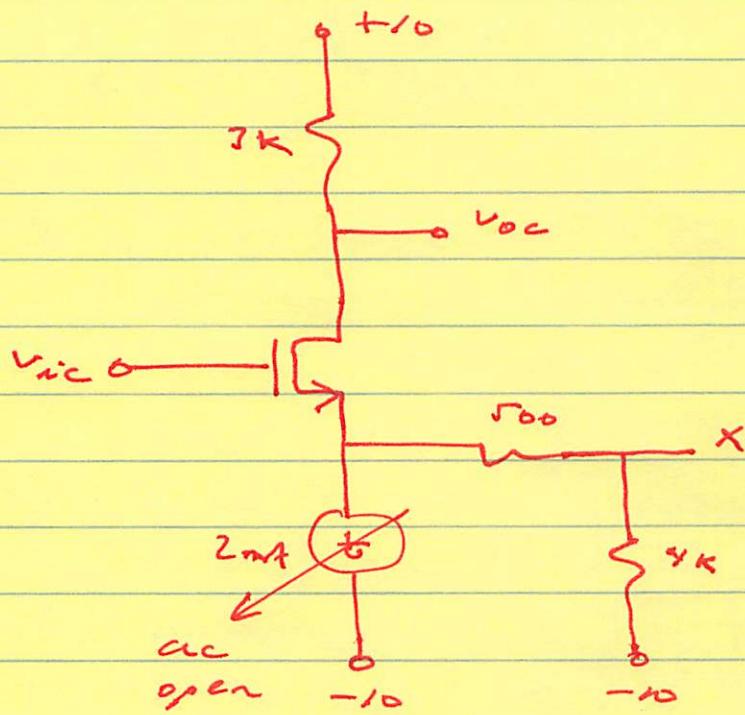

$$Acc = \frac{v_{oc}}{v_{in}} = \frac{-5m(3k)}{1 + 5m(4.5k)} = -0.638$$

9.57

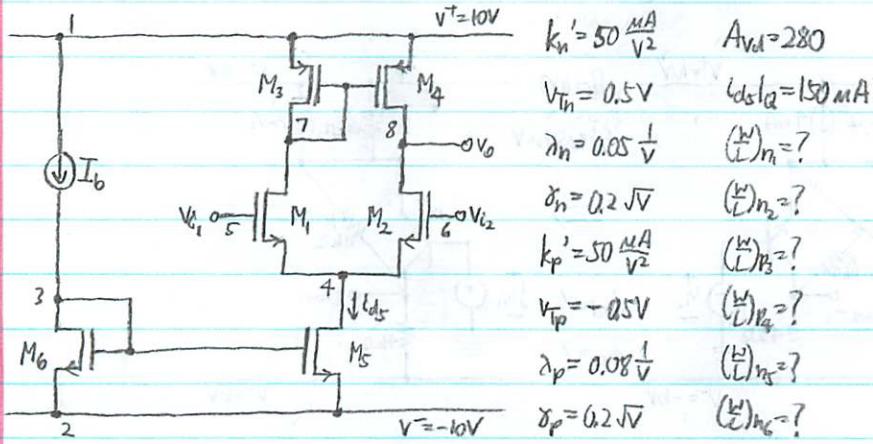

Start w/ crude estimates at 1V so quiescent M₂ source is set at -1V

$$V_{ds2Q} = |V_{ds4Q}| = 5.5V \text{ if quiescent value for } V_O \text{ partitions equal } |V_{ds}| \text{ voltages}$$

$$I_{d2Q} = |I_{d4Q}| = 75 \mu A$$

$$r_{o2} = \frac{\frac{1}{\lambda_n} + |V_{ds1Q}|}{|I_{d2Q}|}, \quad r_{o4} = \frac{\frac{1}{\lambda_p} + |V_{ds3Q}|}{|I_{d4Q}|}, \quad r_{o2} // r_{o4} = \frac{1}{r_{o2}} + \frac{1}{r_{o4}}, \quad A_{vd} = g_m(r_{o2} // r_{o4}), \quad V_{ds5Q} = 9V$$

$$r_{o2} = 3.40 \times 10^5 \Omega, \quad r_{o4} = 2.40 \times 10^5 \Omega, \quad r_{o2} // r_{o4} = 1.41 \times 10^5 \Omega, \quad g_m = \frac{A_{vd}}{r_{o2} // r_{o4}}, \quad V_{ds6Q} = 1V$$

$$g_m = 1.99 \times 10^{-3} \text{ S}$$

$$(\frac{W}{L})_{n_2} = \frac{g_m^2}{2k_n' I_{d2Q} (1 + \lambda_n V_{ds2Q})}, \quad (\frac{W}{L})_{p_1} = (\frac{W}{L})_{p_2} = (\frac{W}{L})_{n_3} = 4 \mu m, \quad (\frac{W}{L})_{n_5} = (\frac{W}{L})_{n_6} = \frac{(1 + \lambda_p V_{ds5Q})}{1 + \lambda_p V_{ds6Q}}$$

$$(\frac{W}{L})_{n_2} = 414.2 \mu m = (\frac{W}{L})_{n_1},$$

$$(\frac{W}{L})_{n_6} = 5.52 \mu m$$

From PSpice simulation, $(\frac{W}{L})_{n_1} = (\frac{W}{L})_{n_2} = 466.1 \mu m$ w/ $A_{vd} = 280.007$ and $I_{d5Q} = 1.99 \times 10^{-4} A$


+ .3

* EE-348L Homework Set 7

```
* Problem 9.57
V+ 1 0 10
V- 2 0 -10
Vi1 5 0 ac 1m
Vi2 0 6 ac 1m
Ib 1 3 dc 150u
M6 3 3 2 2 MOSN W = 5.5u L = 1u
M5 4 3 2 2 MOSN W = 4u L = 1u
M1 7 5 4 4 MOSN W = 466.1u L = 1u
M2 8 6 4 4 MOSN W = 466.1u L = 1u
M3 7 7 1 1 MOSP W = 4u L = 1u
M4 8 7 1 1 MOSP W = 4u L = 1u

.model NMOS NMOS (kp = 50u, VTO = 0.5, LAMBDA = 0.05, GAMMA = 0.2)
.model PMOS PMOS (kp = 20u, VTO = -0.5, LAMBDA = 0.08, GAMMA = 0.2)

.op
.ac dec 100 1k 1G
.probe
.end
```

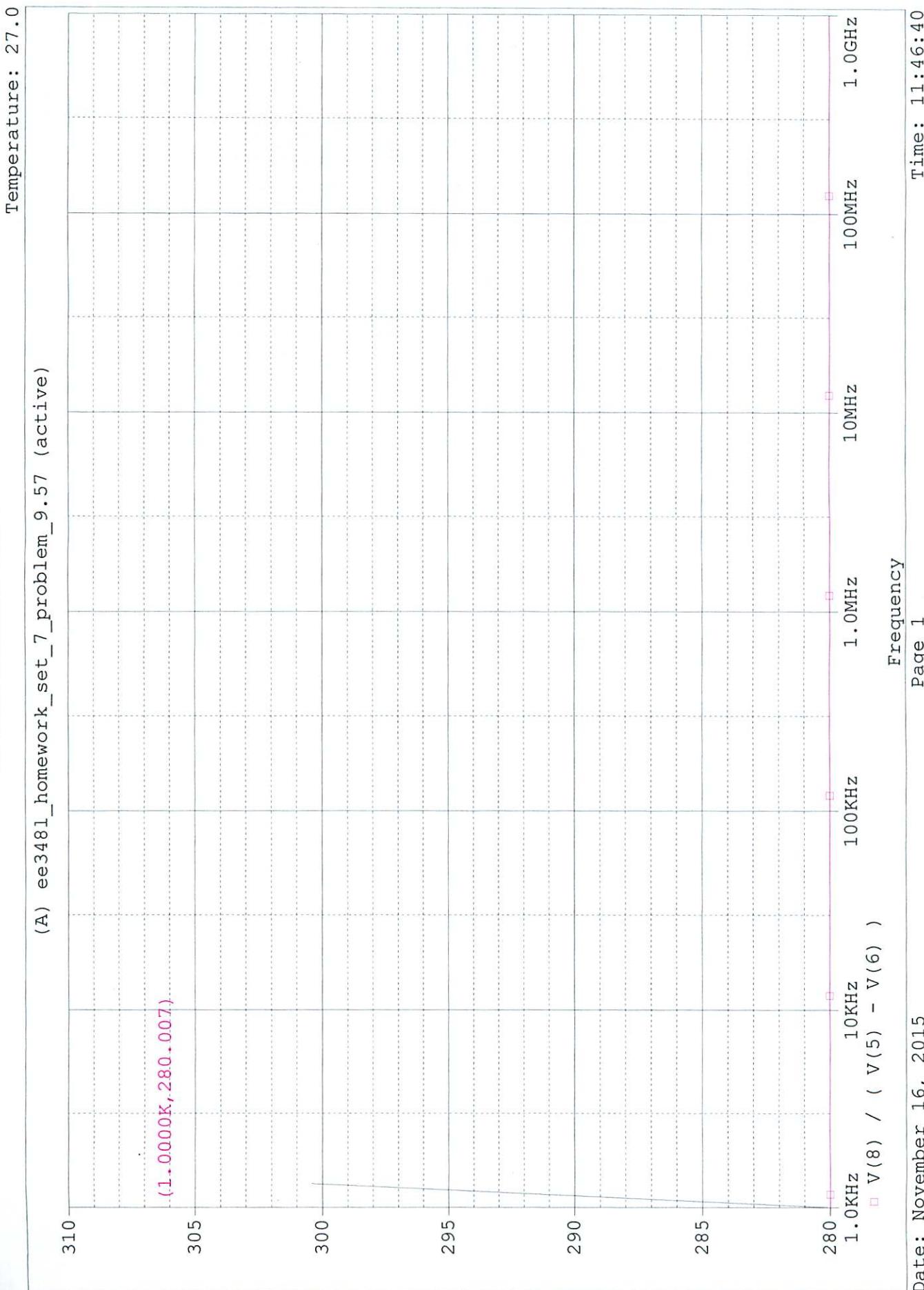

***** 11/16/15 11:46:26 ***** PSpice Lite (October 2012) ***** ID# 10813 *****
* EE-348L Homework Set 7

***** CIRCUIT DESCRIPTION

* Problem 9.57
V+ 1 0 10
V- 2 0 -10
Vi1 5 0 ac 1m
Vi2 0 6 ac 1m
Ib 1 3 dc 150u
M6 3 3 2 2 MOSN W = 5.5u L = 1u
M5 4 3 2 2 MOSN W = 4u L = 1u
M1 7 5 4 4 MOSN W = 466.1u L = 1u
M2 8 6 4 4 MOSN W = 466.1u L = 1u
M3 7 7 1 1 MOSP W = 4u L = 1u
M4 8 7 1 1 MOSP W = 4u L = 1u
.model MOSN NMOS(kp = 50u, VTO = 0.5, LAMBDA = 0.05, GAMMA = 0.2)
.model MOSP PMOS(kp = 20u, VTO = -0.5, LAMBDA = 0.08, GAMMA = 0.2)

.op
.ac dec 100 1k 1G
.probe

.end

***** 11/16/15 11:46:26 ***** PSpice Lite (October 2012) ***** ID# 10813 *****

* EE-348L Homework Set 7

***** MOSFET MODEL PARAMETERS

	MOSN	MOSP
LEVEL	1	1
L	100.000000E-06	100.000000E-06
W	100.000000E-06	100.000000E-06
VTO	.5	-.5
KP	50.000000E-06	20.000000E-06
GAMMA	.2	.2
PHI	.6	.6

LAMBDA	.05	.08
IS	10.000000E-15	10.000000E-15
JS	0	0
PB	.8	.8
PBSW	.8	.8
CJ	0	0
CJSW	0	0
CGSO	0	0
CGDO	0	0
CGBO	0	0
TOX	0	0
XJ	0	0
UCRIT	10.000000E+03	10.000000E+03
DIOMOD	1	1
VFB	0	0
LETA	0	0
WETA	0	0
U0	0	0
TEMP	0	0
VDD	5	5
XPART	0	0

***** 11/16/15 11:46:26 ***** PSpice Lite (October 2012) ***** ID# 10813 *****

* EE-348L Homework Set 7

**** SMALL SIGNAL BIAS SOLUTION TEMPERATURE = 27.000 DEG C

NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE
(1)	10.0000	(2)	-10.0000	(3)	-8.4928	(4)	-.5667
(5)	0.0000	(6)	0.0000	(7)	8.2218	(8)	8.2218

VOLTAGE SOURCE CURRENTS
NAME CURRENT

V+	-2.993E-04
V-	2.993E-04
Vi1	0.000E+00
Vi2	0.000E+00

TOTAL POWER DISSIPATION 5.99E-03 WATTS

***** 11/16/15 11:46:26 ***** PSpice Lite (October 2012) ***** ID# 10813 *****

* EE-348L Homework Set 7

 **** OPERATING POINT INFORMATION TEMPERATURE = 27.000 DEG C

***** MOSFETS

NAME	M6	M5	M1	M2	M3
MODEL	MOSN	MOSN	MOSN	MOSN	MOSP
ID	1.50E-04	1.49E-04	7.46E-05	7.46E-05	-7.46E-05
VGS	1.51E+00	1.51E+00	5.67E-01	5.67E-01	-1.78E+00
VDS	1.51E+00	9.43E+00	8.79E+00	8.79E+00	-1.78E+00
VBS	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00
VTH	5.00E-01	5.00E-01	5.00E-01	5.00E-01	-5.00E-01
VDSAT	1.01E+00	1.01E+00	6.67E-02	6.67E-02	-1.28E+00
Lin0/Sat1	-1.00E+00	-1.00E+00	-1.00E+00	-1.00E+00	-1.00E+00
if	-1.00E+00	-1.00E+00	-1.00E+00	-1.00E+00	-1.00E+00
ir	-1.00E+00	-1.00E+00	-1.00E+00	-1.00E+00	-1.00E+00
TAU	-1.00E+00	-1.00E+00	-1.00E+00	-1.00E+00	-1.00E+00
GM	2.98E-04	2.96E-04	2.24E-03	2.24E-03	1.17E-04
GDS	6.97E-06	5.07E-06	2.59E-06	2.59E-06	5.23E-06
GMB	3.85E-05	3.83E-05	2.89E-04	2.89E-04	1.51E-05
CBD	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00
CBS	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00
CGSOV	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00
CGDOV	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00
CGBOV	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00
CGS	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00
CGD	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00
CGB	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00

NAME	M4
MODEL	MOSP
ID	-7.46E-05
VGS	-1.78E+00
VDS	-1.78E+00
VBS	0.00E+00
VTH	-5.00E-01
VDSAT	-1.28E+00
Lin0/Sat1	-1.00E+00
if	-1.00E+00
ir	-1.00E+00
TAU	-1.00E+00
GM	1.17E-04
GDS	5.23E-06
GMB	1.51E-05
CBD	0.00E+00
CBS	0.00E+00
CGSOV	0.00E+00
CGDOV	0.00E+00
CGBOV	0.00E+00
CGS	0.00E+00
CGD	0.00E+00
CGB	0.00E+00