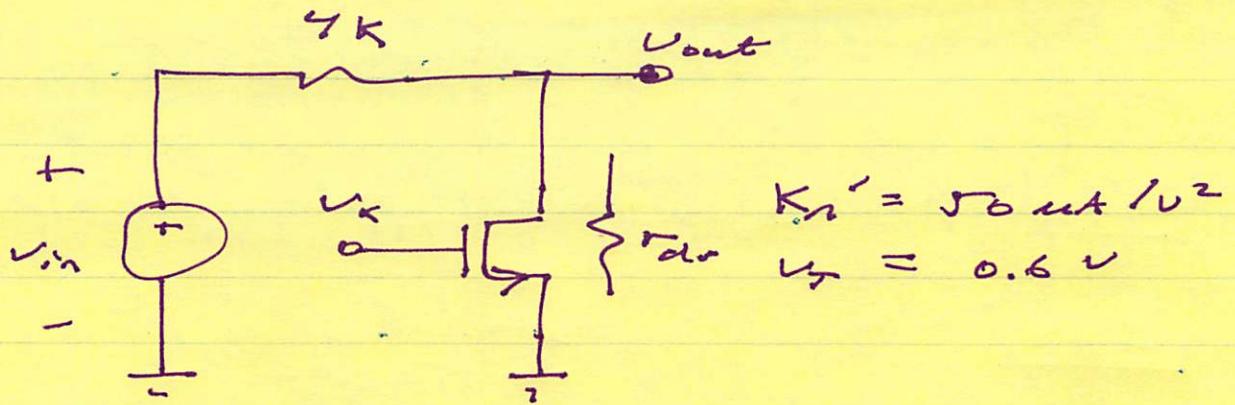


5.29



$$\text{Want } \frac{v_{\text{out}}}{v_{\text{in}}} = 0.1 \text{ for } v_x = v_{\text{in}} = v$$

$$\frac{r_{\text{ds}}}{r_{\text{ds}} + 4k} = \frac{1}{10} \rightarrow r_{\text{ds}} = \frac{4}{9} k$$


$$r_{\text{ds}}^{-1} = 2.25 \times 10^{-2} \text{ } \Omega^{-1}$$

$$\text{But } r_{\text{ds}}^{-1} = K' \frac{w}{L} (v_{\text{gr}} - v_T)$$

$$\rightarrow \frac{w}{L} = \frac{2.25 \times 10^{-2}}{50 \times 10^{-6} \times 4.4}$$

$$= 10.2$$

5.31

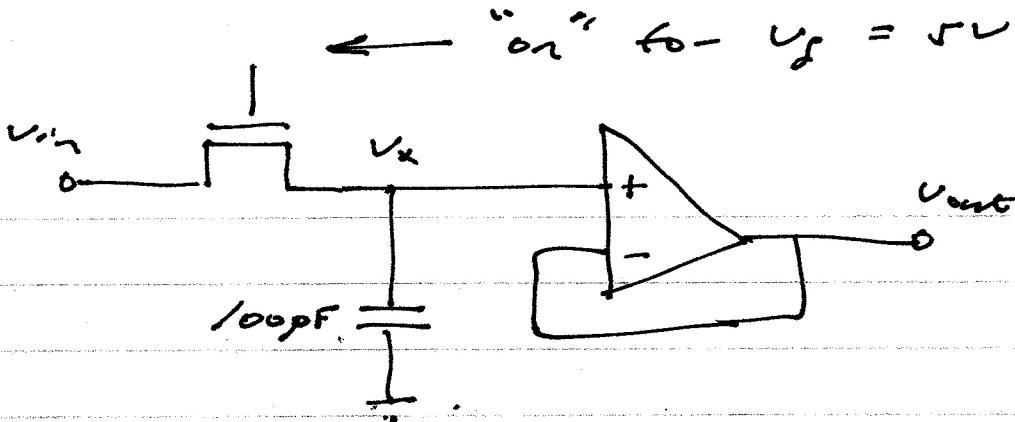

$$K_n' = 50 \text{ nA/V}^2$$

$$V_{TA} = 0.6 \text{ V}$$

a) Let $V_x = 1.024 \text{ V (max)}$

Turn on nMOSFET when $V_{in} = 0 \text{ (min)}$

Assume $1.024/100$ max error.

$$\frac{1}{\sqrt{2}} = \frac{r}{-t} \frac{-t}{nc}$$

$$V_x = 1.024 e$$

$$\text{At } t = 10 \text{ ns, } V_x = \frac{1.024}{100}$$

$$\rightarrow e^{\frac{-t}{nc}} = \frac{1}{100}$$

$$t = nc \ln 100$$

$$r = \frac{10^{-8}}{10^{-10} \ln 100} = 21.7 \text{ n} = \frac{1}{k' \sum (V_{D0} - V_s)}$$


$$\rightarrow \frac{w}{L} = \frac{1}{21.7 \times 50 \times 10^{-6} \times (5 - 0.6)} = 210$$

$$= 210$$

$$V_{pr} = V - 0.5$$

$$r = \frac{1}{K \left(\frac{\omega}{\zeta} \right) (V_{pr} - V_r)}$$

$\Rightarrow \frac{1}{210} \cdot 3.9$

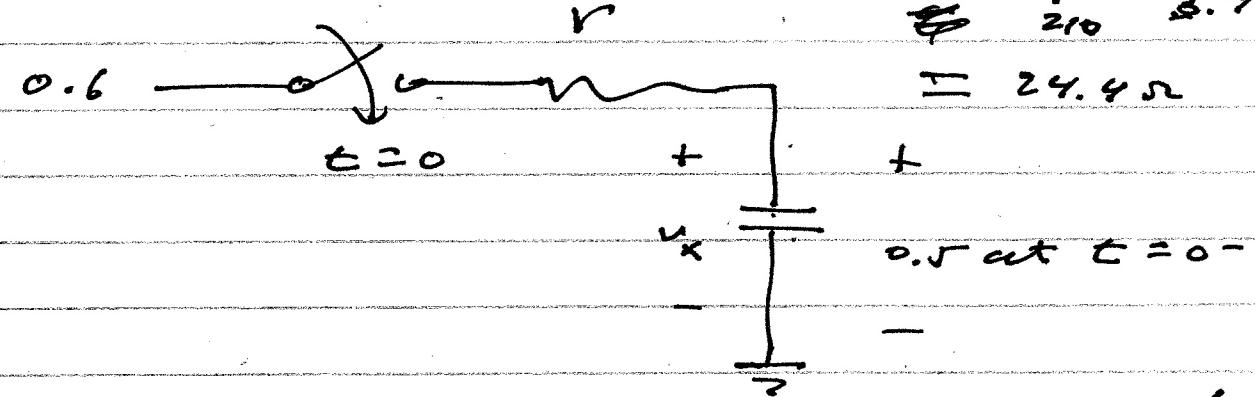


$$v_x = v_x(\infty) + [v_x(0+) - v_x(\infty)] e^{-\frac{t}{rc}}$$

$$= 0.6 - 0.1 e^{-\frac{t}{rc}}$$

$$\text{At } t = 10 \text{ ms}, e^{-\frac{t}{rc}} = 1.66 \times 10^{-2}$$

$$\text{Error} = v_x(10 \text{ ms}) - 0.6 = -1.66 \text{ mV}$$

5.32

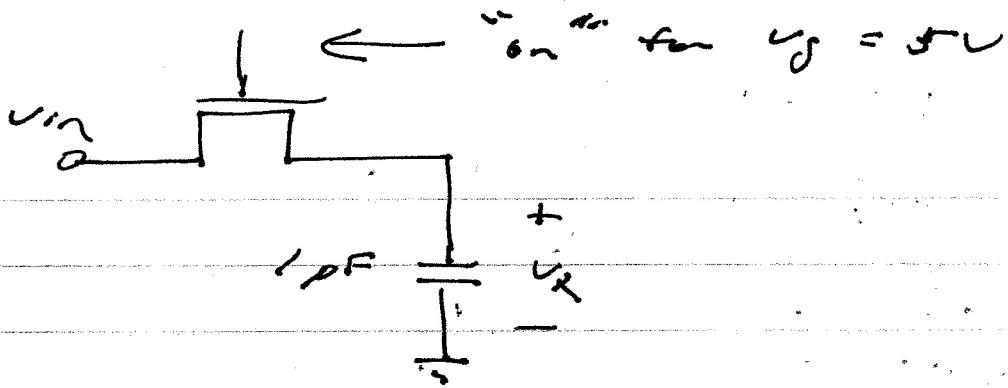

$$K_n' = 65 \text{ mA/V}^2 \quad V_{TN} = 0.6 \text{ V}$$

$$w = 20 \text{ } \mu\text{m}, \quad L = 1.2 \text{ } \mu\text{m}$$

$$C_{ox} = 80 \text{ nF/cm}^2$$

$$V_{DN} = 1 \text{ V} \rightarrow V_{SD} = 5 - 1 = 4 \text{ V}$$

$$V_X \rightarrow 1 \text{ V}$$

$$Q (\text{under gate}) = C_{ox} w L (V_{SD} - V_T)$$


$$= 80 \times 10^{-9} \times 20 \times 10^{-4} \times 1.2 \times 10^{-4} \times 3.4$$

$$= 6.53 \times 10^{-14} \text{ coul}$$

$$\frac{1}{2} Q \rightarrow C$$


$$\Delta V = \frac{\Delta Q}{C} = \frac{3.26 \times 10^{-14}}{10^{-12}} = 32.6 \text{ mV}$$

5.37

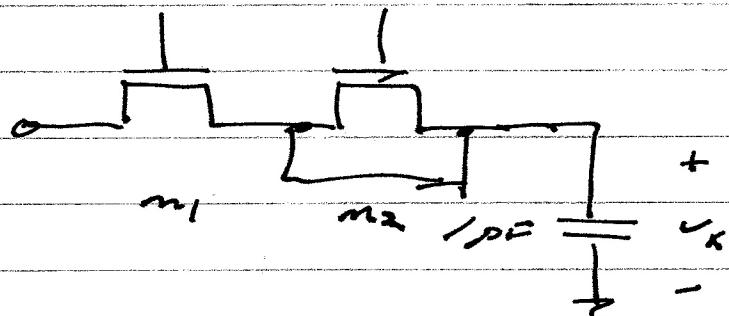

Make $m_2 \frac{w_2}{L_2} = \frac{1}{2} \frac{w_1}{L_1}$ so that m_2 absorbs charge under m_1 ($\frac{1}{2} Q$).

5.47

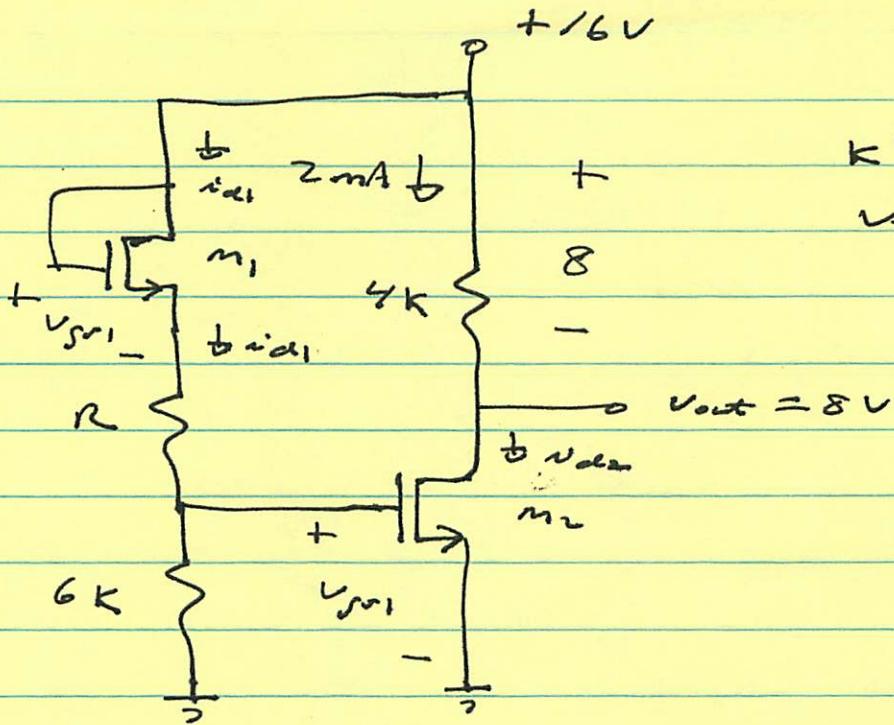

$$K' \frac{v_{ctrl}}{v_{ctrl}} = 1 \text{ mA/V}^2$$

$$v_{ctrl} = 1\text{ V}$$

$$v_{ds2} = 2\text{ mA}$$

$$\hookrightarrow 2 = \frac{1}{2}(1)(v_{ctrl} - 1)^2 \rightarrow v_{ctrl} = 3, \cancel{\text{X}}$$

$$\rightarrow n_{d1} = \frac{3}{6\text{ k}} = 0.5\text{ mA}$$


~~$$0.5 = \frac{1}{2}(1)(v_{in1} - 1)^2 \rightarrow v_{in1} = 2, \cancel{\text{X}}$$~~

$$\hookrightarrow r = \frac{(16 - 2) - 2}{0.5} = \underline{22\text{ k}}$$

5. 84

$$K' \frac{C}{V} = 2mA/V^2$$

$$C_f = -1\text{nF}$$

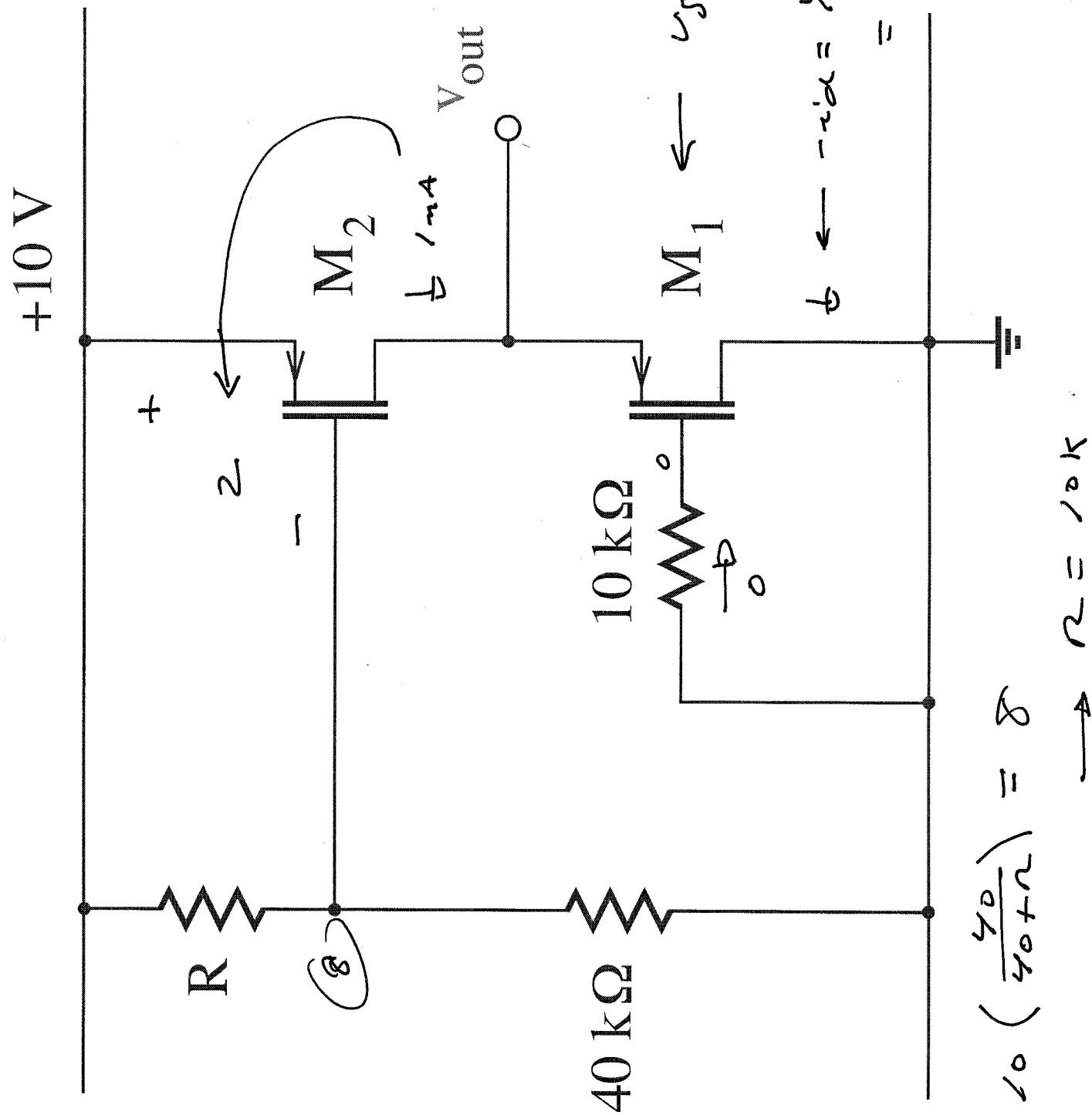


$$5.45 \quad m_1 : k_n' \frac{w}{l} = 2mA/V^2, V_T = 1V$$

$$m_2 : k_p' \frac{w}{l} = 0.25mA/V^2, V_T = -1V$$

$$m_1 \rightarrow id_1 = 1 = \frac{1}{2}(z)(v_{gs} - 1)^2 \rightarrow v_{gs} = 2V$$

~~$v_{gs} \leq 0V$~~

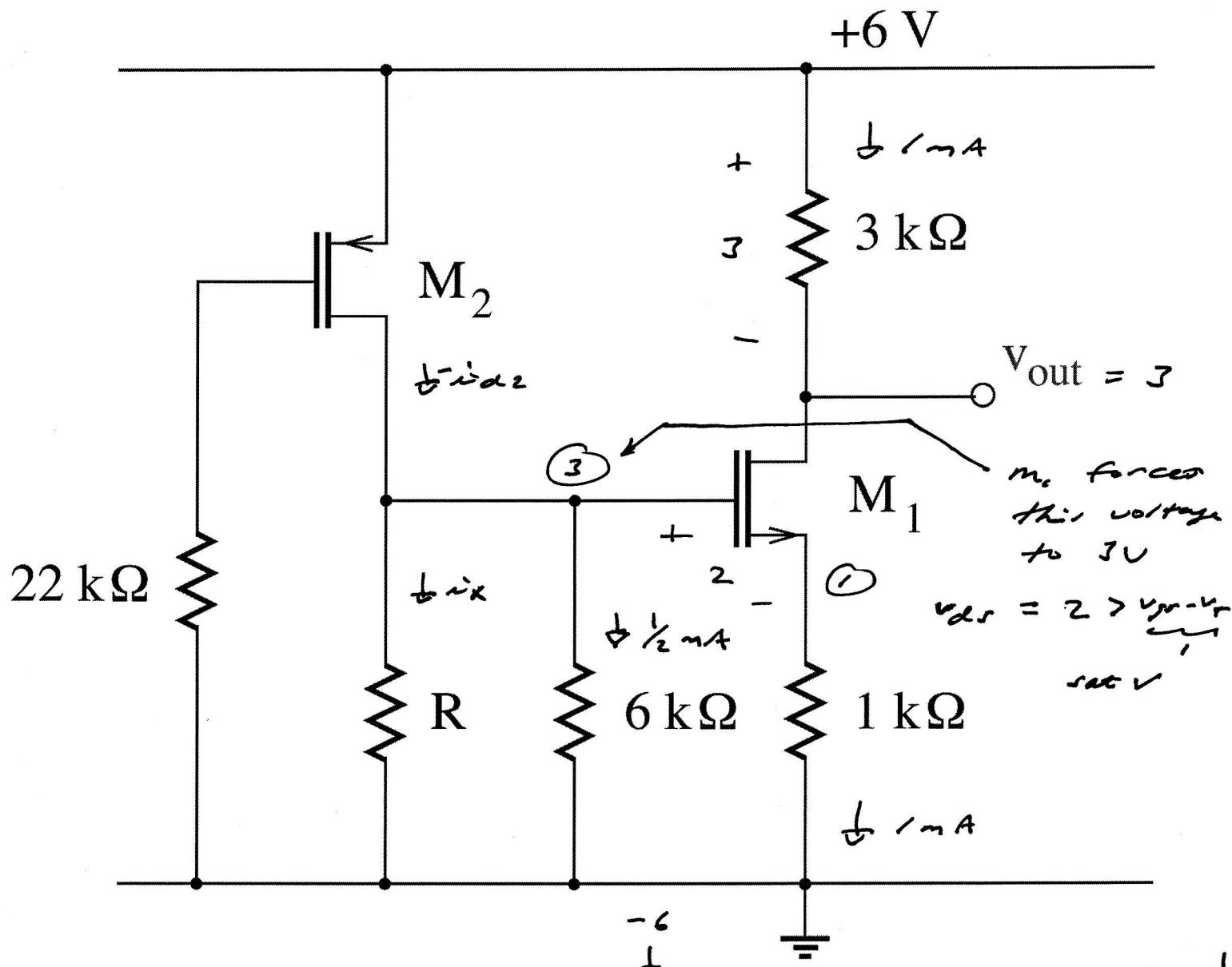

$$m_2 : v_{ds} = -3 \Rightarrow v_{gs} - v_T = -5 \quad \text{negative!}$$

$$-id_2 = \frac{1}{2}k_p' \frac{w}{l} \underbrace{\left[2(v_{gs} - v_T)v_{ds} - v_{ds}^2 \right]}_{21} = 2.625mA$$

$$\rightarrow i_x = 2.125mA$$

$$R = \frac{3}{2.125} = \underline{1.41k}$$

5. 46

$$K \cdot \frac{U_2}{U_1} = 2 \text{ mA} / 1 \text{ mA}$$

+10 V

$$R = \frac{10 - 2}{1} = \frac{8 \text{ k}}{\text{A}}$$

R

2 kΩ

V_{out} = 6

1 kΩ

↓ 1 mA

↓ 1 mA

M₂

M₃

↓ 1 mA

M₁

2
-

$$r = r_2 (z) (v_{DD} - v)^2$$

$$v_{DD} = 2, \quad v_{DD1} = 2 > 2 - 1$$

same v_{DD}

✓