

University of Southern California
Ming Hsieh Department of Electrical Engineering
EE 348L - Electronic Circuits
Spring 2016

Homework 1 Solutions

1.1 (a) $I = \frac{V}{R} = \frac{5 \text{ V}}{1 \text{ k}\Omega} = 5 \text{ mA}$

(b) $R = \frac{V}{I} = \frac{5 \text{ V}}{1 \text{ mA}} = 5 \text{ k}\Omega$

(c) $V = IR = 0.1 \text{ mA} \times 10 \text{ k}\Omega = 1 \text{ V}$

(d) $I = \frac{V}{R} = \frac{1 \text{ V}}{100 \Omega} = 0.01 \text{ A} = 10 \text{ mA}$

Note: Volts, milliamps, and kilohms constitute a consistent set of units.

1.3 (a) $V = IR = 5 \text{ mA} \times 1 \text{ k}\Omega = 5 \text{ V}$

$$P = I^2 R = (5 \text{ mA})^2 \times 1 \text{ k}\Omega = 25 \text{ mW}$$

(b) $R = V/I = 5 \text{ V}/1 \text{ mA} = 5 \text{ k}\Omega$

$$P = VI = 5 \text{ V} \times 1 \text{ mA} = 5 \text{ mW}$$

(c) $I = P/V = 100 \text{ mW}/10 \text{ V} = 10 \text{ mA}$

$$R = V/I = 10 \text{ V}/10 \text{ mA} = 1 \text{ k}\Omega$$

(d) $V = P/I = 1 \text{ mW}/0.1 \text{ mA}$

$$= 10 \text{ V}$$

$$R = V/I = 10 \text{ V}/0.1 \text{ mA} = 100 \text{ k}\Omega$$

(e) $P = I^2 R \Rightarrow I = \sqrt{P/R}$

$$I = \sqrt{1000 \text{ mW}/1 \text{ k}\Omega} = 31.6 \text{ mA}$$

$$V = IR = 31.6 \text{ mA} \times 1 \text{ k}\Omega = 31.6 \text{ V}$$

Note: V, mA, k Ω , and mW constitute a consistent set of units.

Done

1.7 Use voltage divider to find V_O

$$V_O = 5 \frac{2}{2+3} = 2 \text{ V}$$

Equivalent output resistance R_O is

$$R_O = (2 \text{ k}\Omega \parallel 3 \text{ k}\Omega) = 1.2 \text{ k}\Omega$$


The extreme values of V_O for $\pm 5\%$ tolerance resistor are

$$V_{O\min} = 5 \frac{2(1 - 0.05)}{2(1 - 0.05) + 3(1 + 0.05)}$$

$$= 1.88 \text{ V}$$

$$V_{O\max} = 5 \frac{2(1 + 0.05)}{2(1 + 0.05) + 3(1 - 0.05)}$$


$$= 2.12 \text{ V}$$

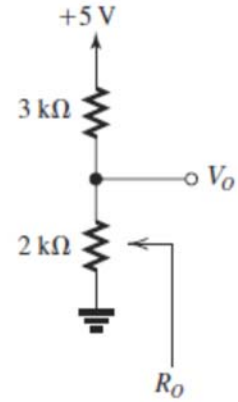



The extreme values of R_O for $\pm 5\%$ tolerance resistors are $1.2 \times 1.05 = 1.26 \text{ k}\Omega$ and $1.2 \times 0.95 = 1.14 \text{ k}\Omega$.

Done

1.15

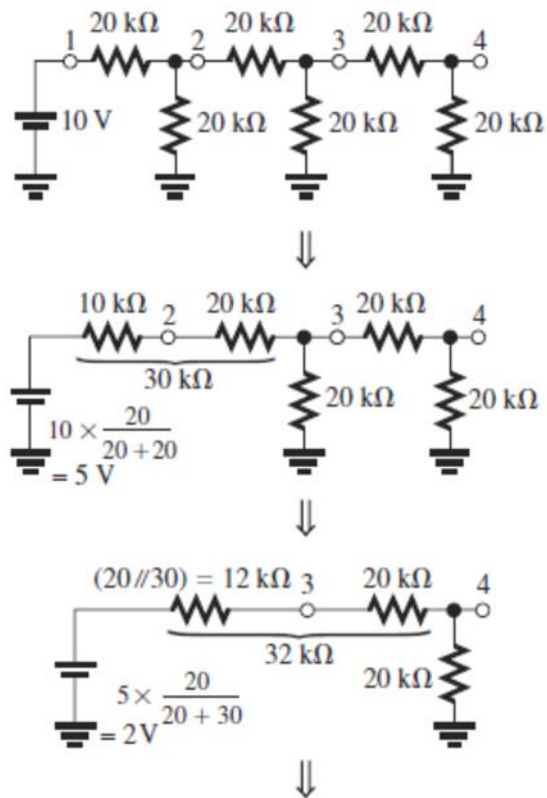

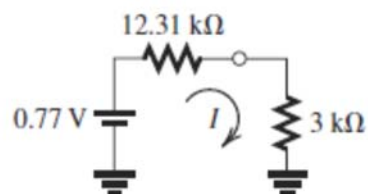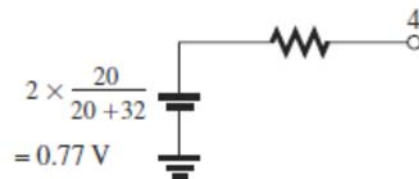Thévenin equivalent: $(20 // 32) = 12.31 \text{ k}\Omega$



Now, when a resistance of $3 \text{ k}\Omega$ is connected between node 4 and ground,

$$I = \frac{0.77}{12.31 + 3}$$

$$= 0.05 \text{ mA}$$

Done

1.19 Refer to Fig. P1.19. Using the voltage divider rule at the input side, we obtain

$$\frac{v_{\pi}}{v_s} = \frac{r_{\pi}}{r_{\pi} + R_s} \quad (1)$$

At the output side, we find v_o by multiplying the current $g_m v_{\pi}$ by the parallel equivalent of r_o and R_L ,

$$v_o = -g_m v_{\pi} (r_o \parallel R_L) \quad (2)$$

Finally, v_o/v_s can be obtained by combining Eqs. (1) and (2) as

$$\frac{v_o}{v_s} = -\frac{r_{\pi}}{r_{\pi} + R_s} g_m (r_o \parallel R_L)$$

Done

1.28

Case	ω (rad/s)	f (Hz)	T (s)
a	3.14×10^{10}	5×10^9	0.2×10^{-9}
b	2×10^9	3.18×10^8	3.14×10^{-9}
c	6.28×10^{10}	1×10^{10}	1×10^{-10}
d	3.77×10^2	60	1.67×10^{-2}
e	6.28×10^4	1×10^4	1×10^{-4}
f	6.28×10^5	1×10^5	1×10^{-5}

Done

$$1.39 \text{ (a) } A_v = \frac{v_O}{v_I} = \frac{10 \text{ V}}{100 \text{ mV}} = 100 \text{ V/V}$$

$$\text{or } 20 \log 100 = 40 \text{ dB}$$

$$A_i = \frac{i_O}{i_I} = \frac{v_O/R_L}{i_I} = \frac{10 \text{ V}/100 \Omega}{100 \mu\text{A}} = \frac{0.1 \text{ A}}{100 \mu\text{A}}$$
$$= 1000 \text{ A/A}$$

$$\text{or } 20 \log 1000 = 60 \text{ dB}$$

$$A_p = \frac{v_O i_O}{v_I i_I} = \frac{v_O}{v_I} \times \frac{i_O}{i_I} = 100 \times 1000$$
$$= 10^5 \text{ W/W}$$

$$\text{or } 10 \log 10^5 = 50 \text{ dB}$$

$$\text{(b) } A_v = \frac{v_O}{v_I} = \frac{1 \text{ V}}{10 \mu\text{V}} = 1 \times 10^5 \text{ V/V}$$

$$\text{or } 20 \log 1 \times 10^5 = 100 \text{ dB}$$

$$A_i = \frac{i_O}{i_I} = \frac{v_O/R_L}{i_I} = \frac{1 \text{ V}/10 \text{ k}\Omega}{100 \text{ nA}}$$
$$= \frac{0.1 \text{ mA}}{100 \text{ nA}} = \frac{0.1 \times 10^{-3}}{100 \times 10^{-9}} = 1000 \text{ A/A}$$

$$\text{or } 20 \log A_i = 60 \text{ dB}$$

$$A_p = \frac{v_O i_O}{v_I i_I} = \frac{v_O}{v_I} \times \frac{i_O}{i_I}$$
$$= 1 \times 10^5 \times 1000$$
$$= 1 \times 10^8 \text{ W/W}$$

$$\text{or } 10 \log A_p = 80 \text{ dB}$$

$$\text{(c) } A_v = \frac{v_O}{v_i} = \frac{5 \text{ V}}{1 \text{ V}} = 5 \text{ V/V}$$

$$\text{or } 20 \log 5 = 14 \text{ dB}$$

$$A_i = \frac{i_o}{i_I} = \frac{v_o/R_L}{i_I} = \frac{5 \text{ V}/10 \text{ } \Omega}{1 \text{ mA}}$$

$$= \frac{0.5 \text{ A}}{1 \text{ mA}} = 500 \text{ A/A}$$

$$\text{or } 20 \log 500 = 54 \text{ dB}$$


$$A_p = \frac{v_o i_o}{v_I i_I} = \frac{v_o}{v_I} \times \frac{i_o}{i_I}$$

$$= 5 \times 500 = 2500 \text{ W/W}$$

$$\text{or } 10 \log A_p = 34 \text{ dB}$$

Done
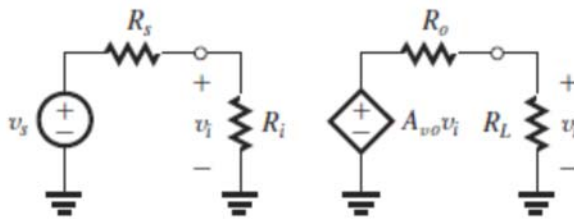
$$\begin{aligned} 1.43 \quad v_o &= A_{vo} v_i \frac{R_L}{R_L + R_o} \\ &= A_{vo} \left(v_s \frac{R_i}{R_i + R_s} \right) \frac{R_L}{R_L + R_o} \end{aligned}$$



Thus,

$$\frac{v_o}{v_s} = A_{vo} \frac{R_i}{R_i + R_s} \frac{R_L}{R_L + R_o}$$

$$(a) \quad A_{vo} = 100, R_i = 10R_s, R_L = 10R_o:$$

$$\begin{aligned} \frac{v_o}{v_s} &= 100 \times \frac{10R_s}{10R_s + R_s} \times \frac{10R_o}{10R_o + R_o} \\ &= 82.6 \text{ V/V or } 20 \log 82.6 = 38.3 \text{ dB} \end{aligned}$$

$$(b) \quad A_{vo} = 100, R_i = R_s, R_L = R_o:$$

$$\frac{v_o}{v_s} = 100 \times \frac{1}{2} \times \frac{1}{2} = 25 \text{ V/V or } 20 \log 25 = 28 \text{ dB}$$


$$(c) \quad A_{vo} = 100 \text{ V/V}, R_i = R_s/10, R_L = R_o/10:$$

$$\begin{aligned} \frac{v_o}{v_s} &= 100 \frac{R_s/10}{(R_s/10) + R_s} \frac{R_o/10}{(R_o/10) + R_o} \\ &= 0.826 \text{ V/V or } 20 \log 0.826 = -1.7 \text{ dB} \end{aligned}$$

Done


1.71 The given measured data indicate that this amplifier has a low-pass STC frequency response with a low-frequency gain of 40 dB, and a 3-dB frequency of 10^4 Hz. From our knowledge of the Bode plots for low-pass STC networks [Fig. 1.23(a)], we can complete the table entries and sketch the amplifier frequency response.

f (Hz)	$ T $ (dB)	$\angle T$ ($^\circ$)
0	40	0
100	40	0
1000	40	0
10^4	37	-45°
10^5	20	-90°
10^6	0	-90°

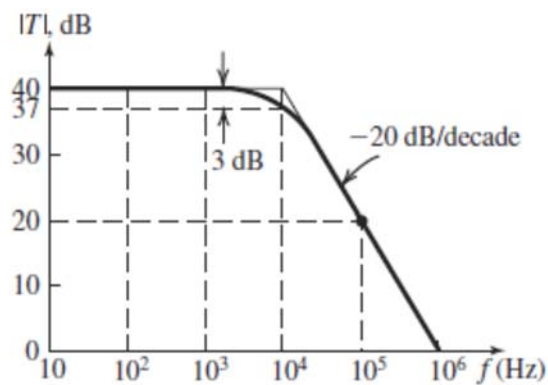

Done

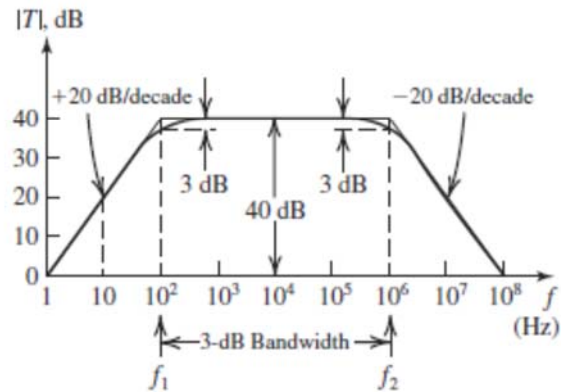1.72 From our knowledge of the Bode plots of STC low-pass and high-pass networks, we see that this amplifier has a midband gain of 40 dB, a low-frequency response of the high-pass STC type with $f_{3\text{dB}} = 10^2$ Hz, and a high-frequency response of the low-pass STC type with $f_{3\text{dB}} = 10^6$ Hz. We thus can sketch the amplifier frequency response and complete the table entries as follows.



f (Hz)	1	10	10^2	10^3	10^4	10^5	10^6	10^7	10^8
$ T $ (dB)	0	20	37	40	40	40	37	20	0