

University of Southern California

Ming Hsieh Department of Electrical Engineering

EE 348L - Electronic Circuits

Homework Set #8

Due in class, Friday, 4 December

Reading - Sections 11.1, 11.2, 12.1, 12.2

Problems 11.8, 11.20, 12.12, 12.30 (solve for $\phi = 45^\circ$ and $\phi = 70^\circ$)